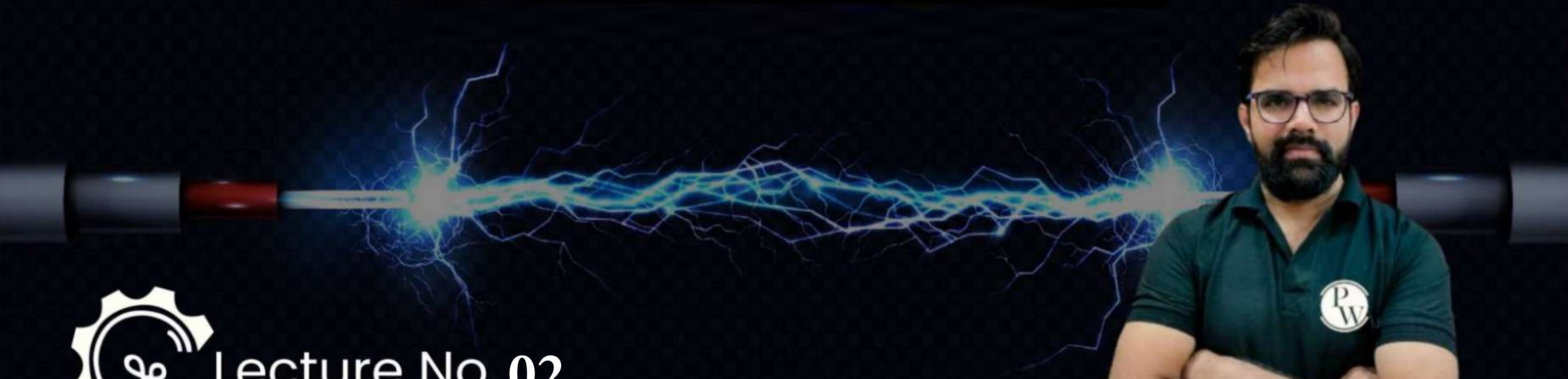


# Electrical Engineering

Electronics and Communication Engineering

## NETWORK THEORY



Lecture No. 02

**BASICS OF**

**NETWORK THEORY**

By- Pankaj Shukla sir





# Topics to be Covered

1. Basics

2. KVL & KCL

3. Sources

4.

5.

6.




$$\left[ \begin{array}{l} P_{\text{absorb}} = \oplus \text{ or } \ominus \longrightarrow P_{\text{Actual absorb}} = \oplus \\ P_{\text{deliver}} = \oplus \text{ or } \ominus \longrightarrow P_{\text{Actual Deliver}} = \oplus \end{array} \right]$$

$$P_{\text{deliver}} = \oplus \text{ or } \ominus$$

GATE

$$P_{\text{Actual Deliver}} = \oplus$$

GATE

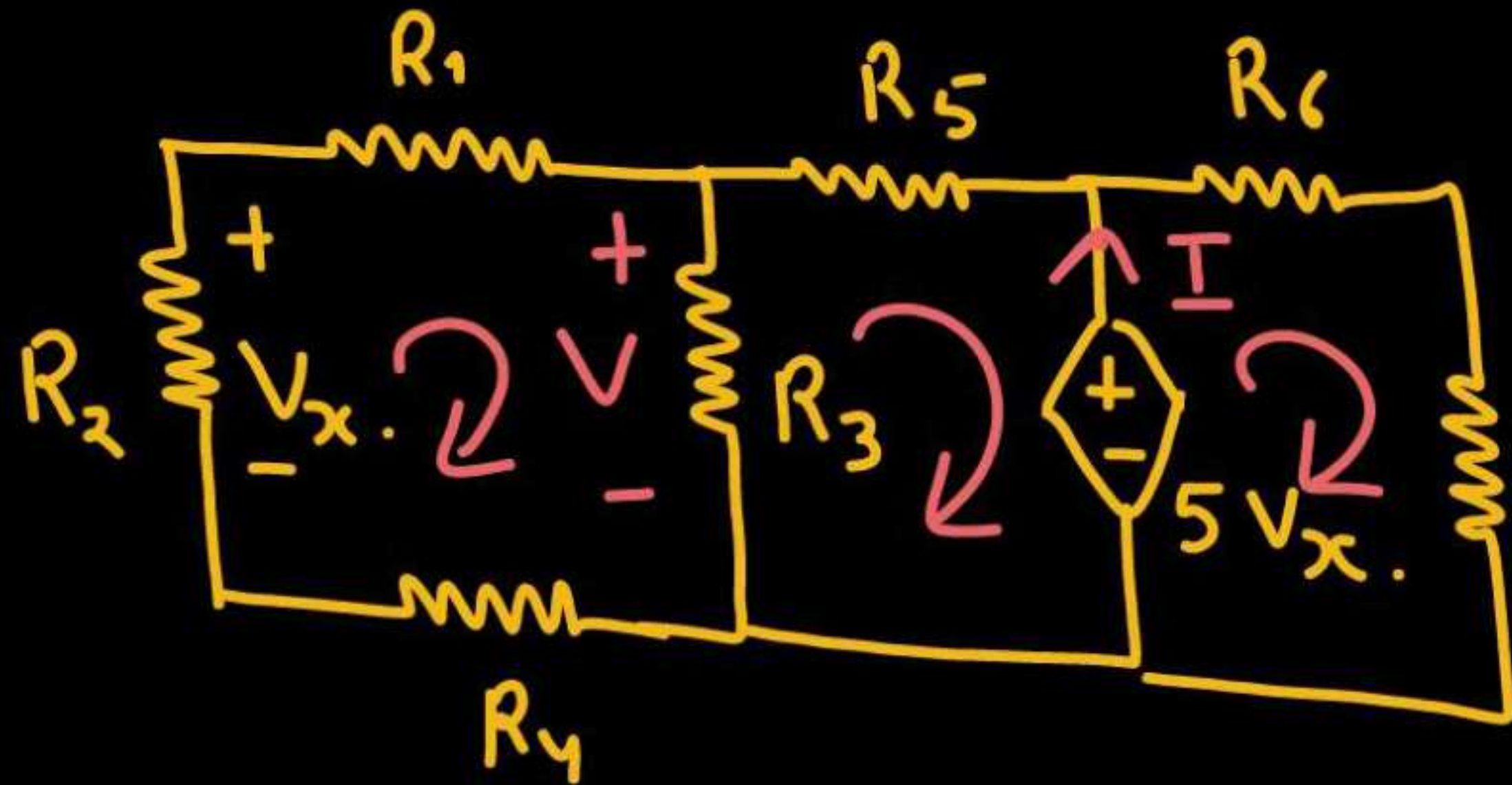

current flow  $\rightarrow$ .

cond<sup>h</sup> 1  $\rightarrow$  X


cond<sup>h</sup> 2  $\rightarrow$  ✓

cond<sup>h</sup> 3  $\rightarrow$  ✓


[current = 0 A]

(Dead circuit) N/A



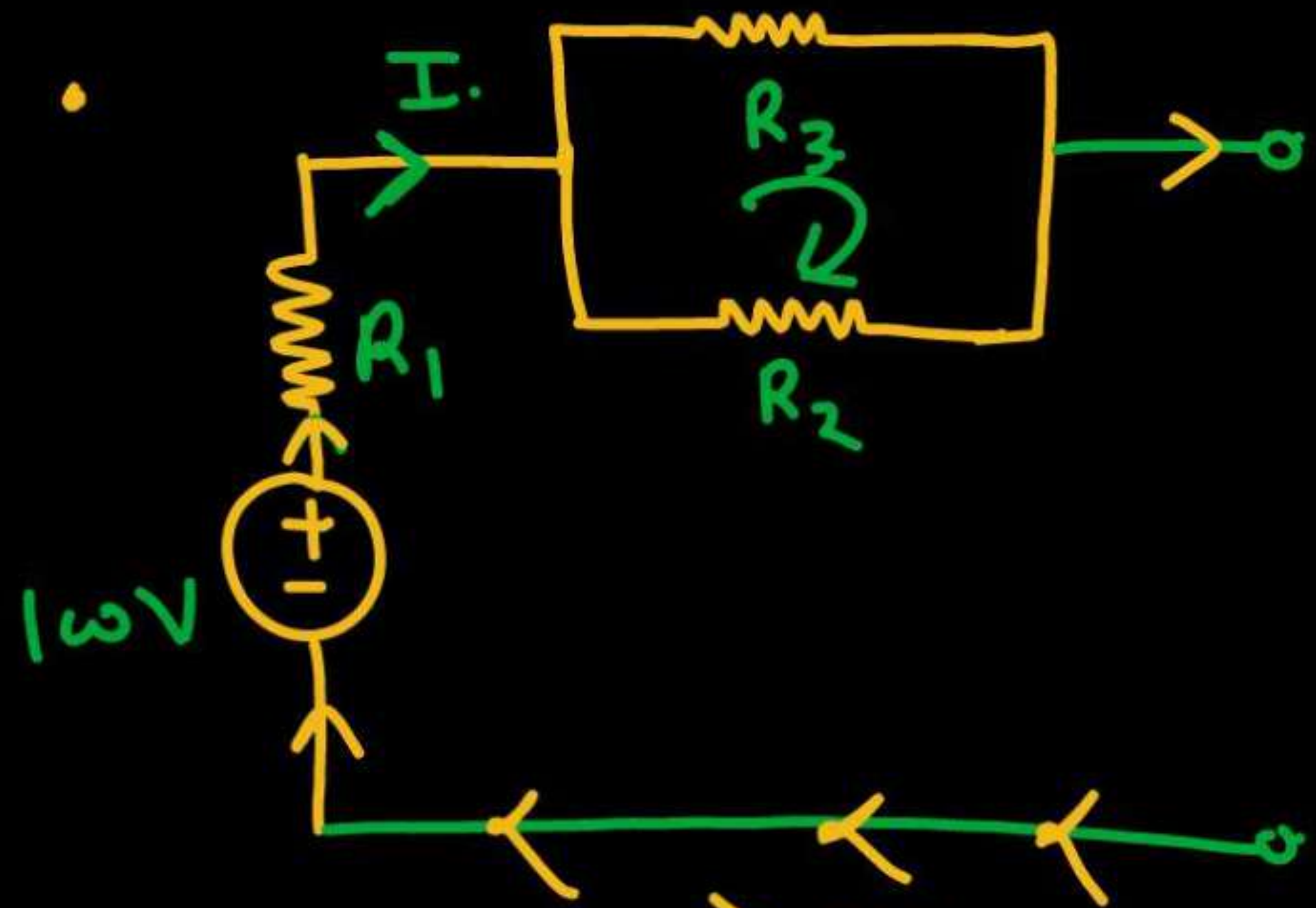


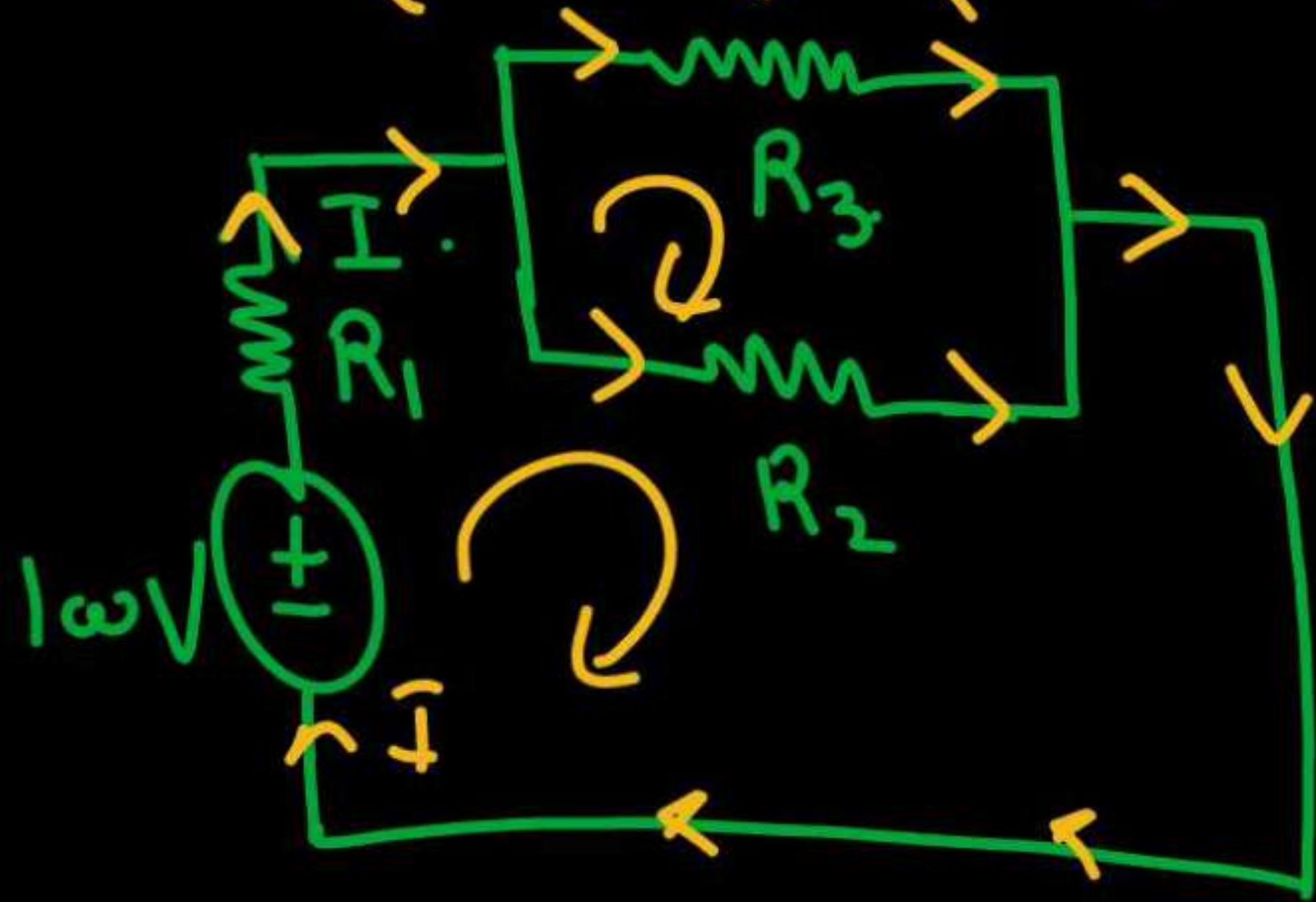$\text{cand}^h 1 \rightarrow \checkmark$   
 $\text{cand}^h 2 \rightarrow \checkmark$   
 $\text{cand}^h 3 \rightarrow \times$   
 $I = 0A$   
 (Dead circuit).



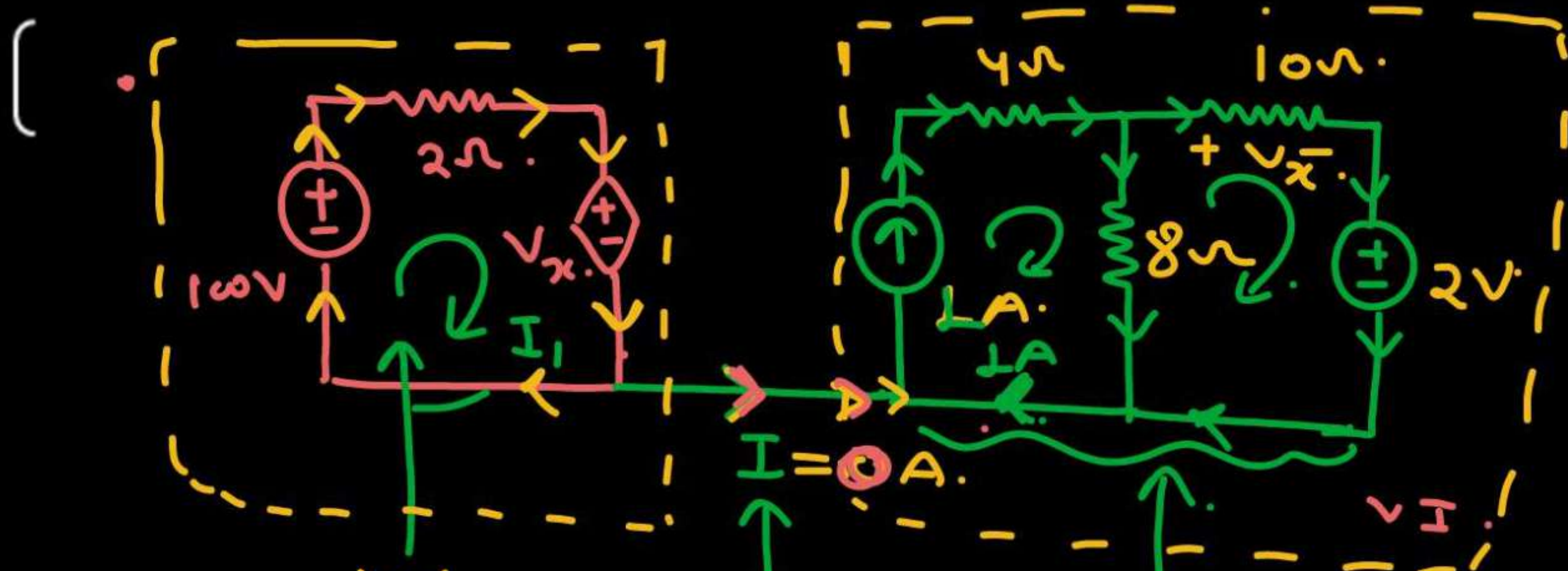$\text{cand}^h 1 \rightarrow \checkmark$   
 $\text{cand}^h 2 \rightarrow \checkmark$   
 $\text{cand}^h 3 \rightarrow \checkmark$   
 $(I \neq 0A)$  (Active circuit)







$N/w A.$   
 $\downarrow$   
 $Cond^h 1 \rightarrow \checkmark$   
 $Cond^h 2 \rightarrow \checkmark$   
 $Cond^h 3 \rightarrow \checkmark$   
 $(I \neq 0A)$

$Cond^h 1 \rightarrow \checkmark$   
 $Cond^h 2 \rightarrow \checkmark$   
 $Cond^h 3 \rightarrow X$   
 $I = 0A$

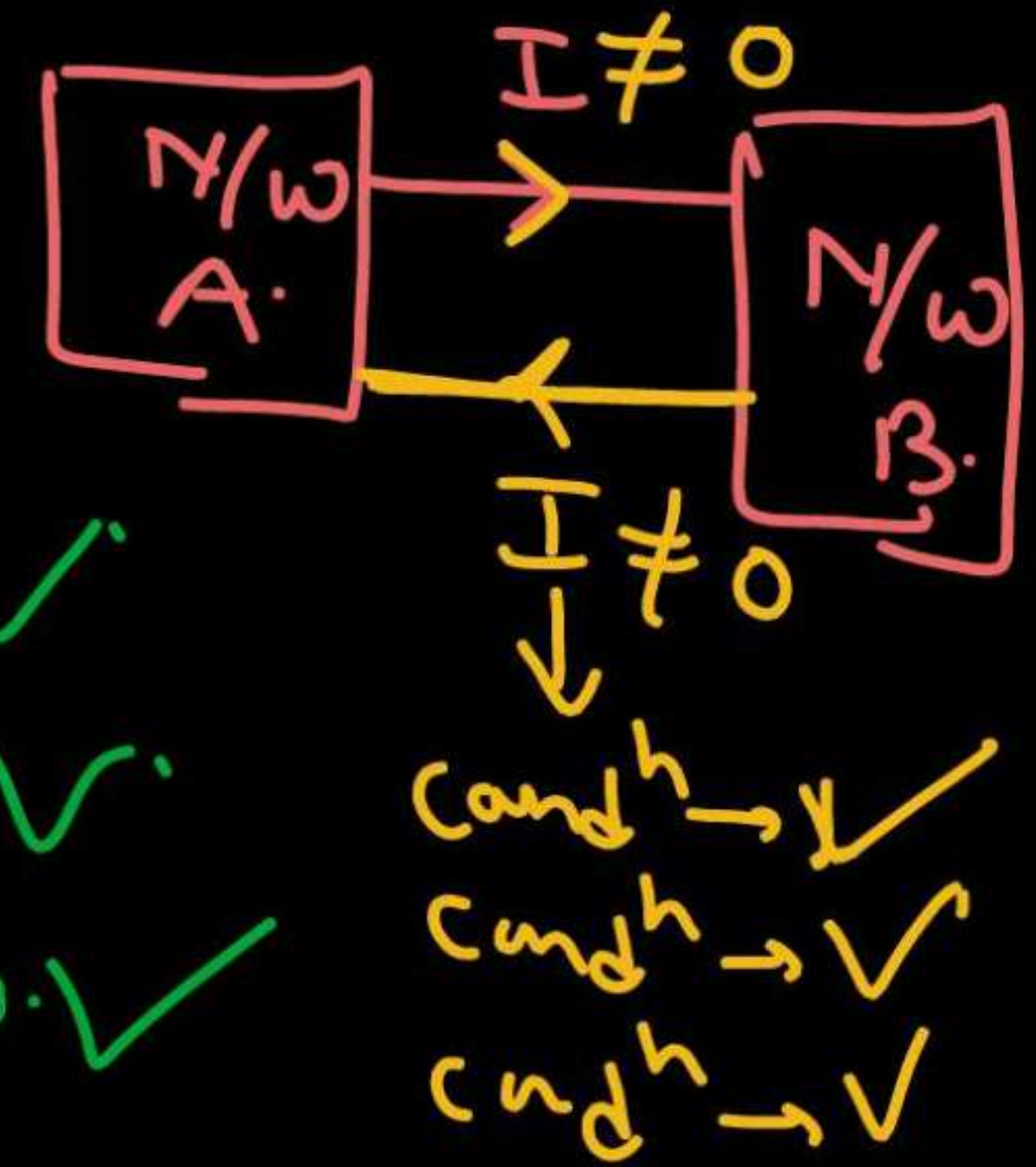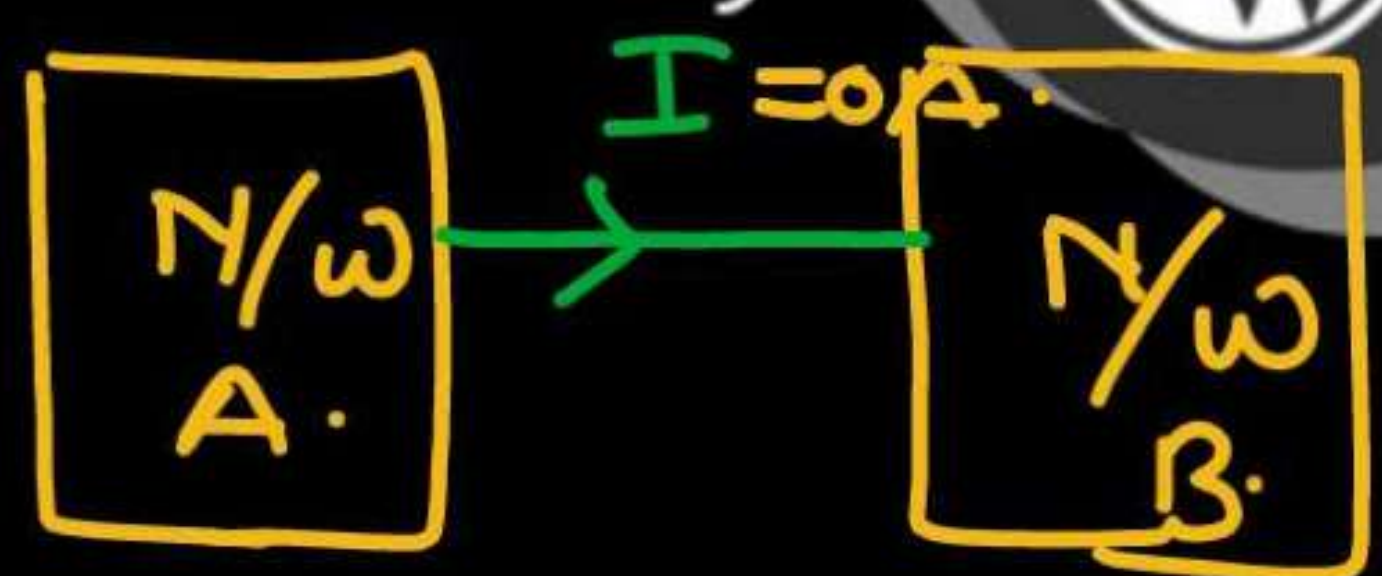$N/w B$   
 $\downarrow$   
 $Cond^h 1 \rightarrow \checkmark$   
 $Cond^h 2 \rightarrow \checkmark$   
 $Cond^h 3 \rightarrow \checkmark$





• Ohm's law, KVL & KCL → Topic-(03)

(1) Ohm's law →

(a)  $V \propto I$   
or


$V = (R) I$  ✓  
Resistance ( $\Omega$ )

$x = R \cdot y$   
 $y = \left(\frac{1}{R}\right) \cdot x$

(b)  $I \propto V$

$I = \left(\frac{1}{R}\right) \cdot V = G \cdot V$  ✓  
Conductance ( $S$ )  
 $y = \left(\frac{1}{R}\right) \cdot x$

I-y-axis.

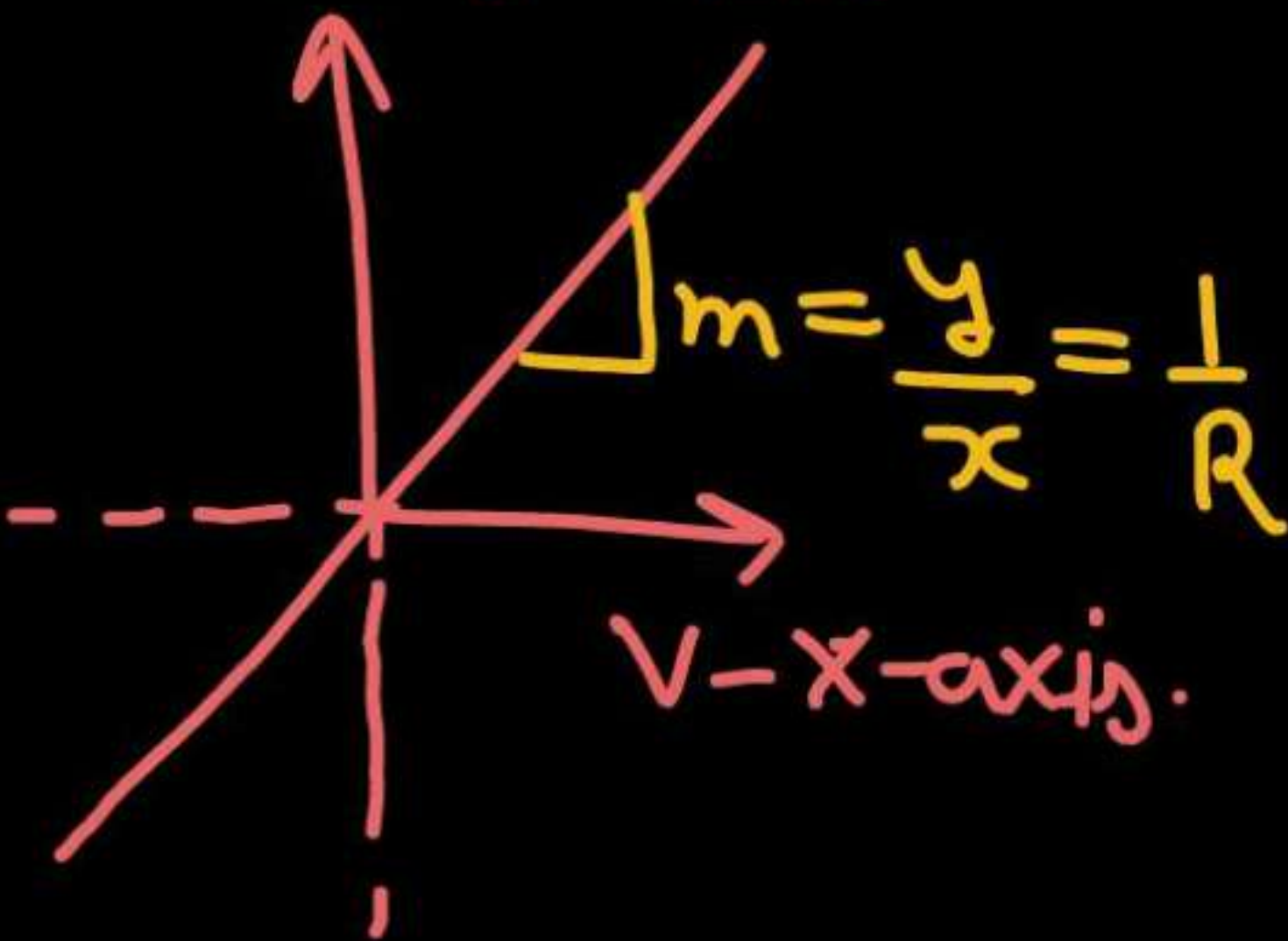

V-x-axis.

$[y = m \cdot x]$


$m = \frac{1}{R} = \left(\frac{y}{x}\right)$

→ equation of a straight line passing through the origin.




[ Case-I Now if we increase the slope ( $m = \frac{1}{R} \Rightarrow \uparrow \uparrow$  )
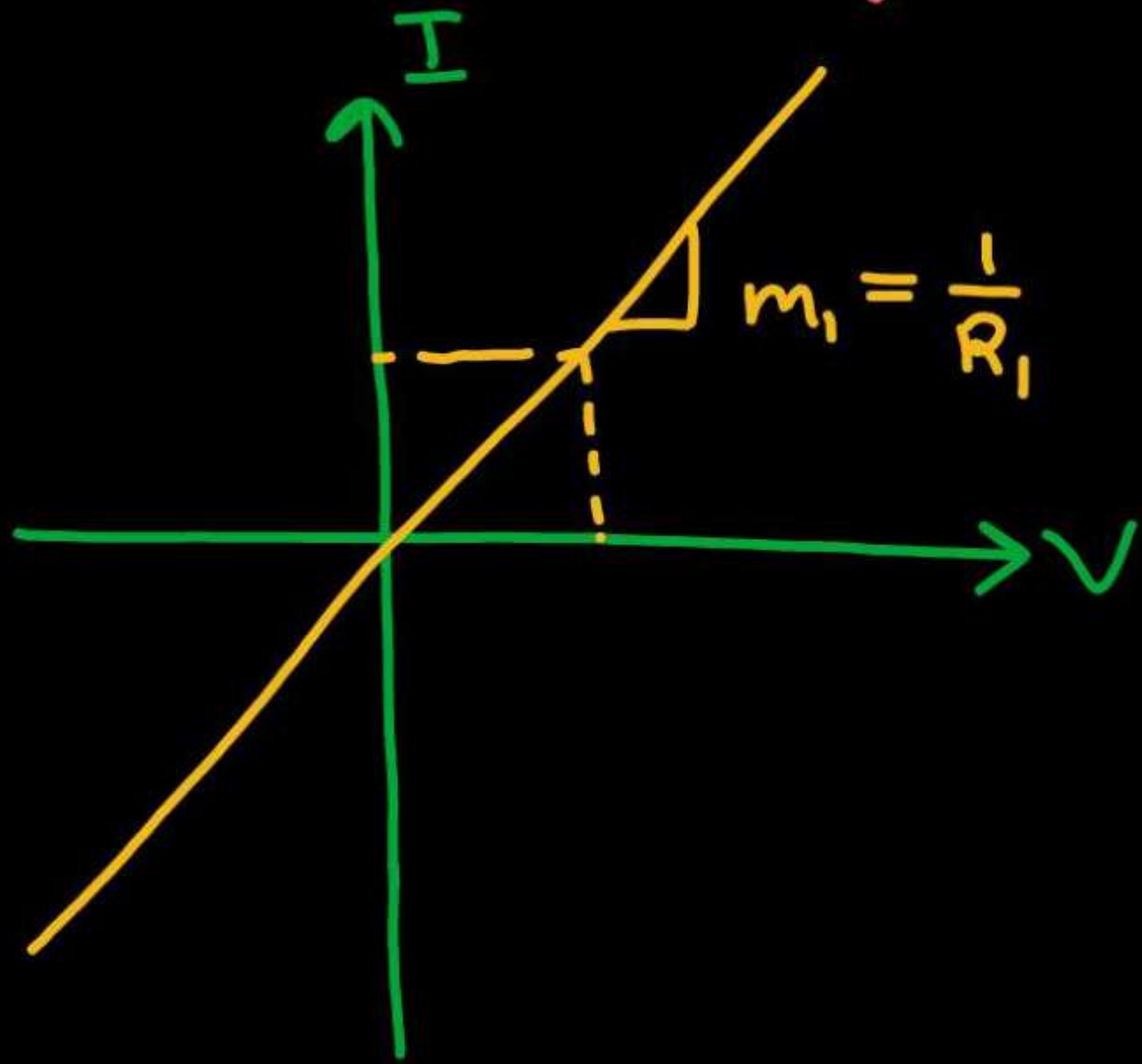
$$\uparrow m = \frac{\uparrow y}{\downarrow x}$$





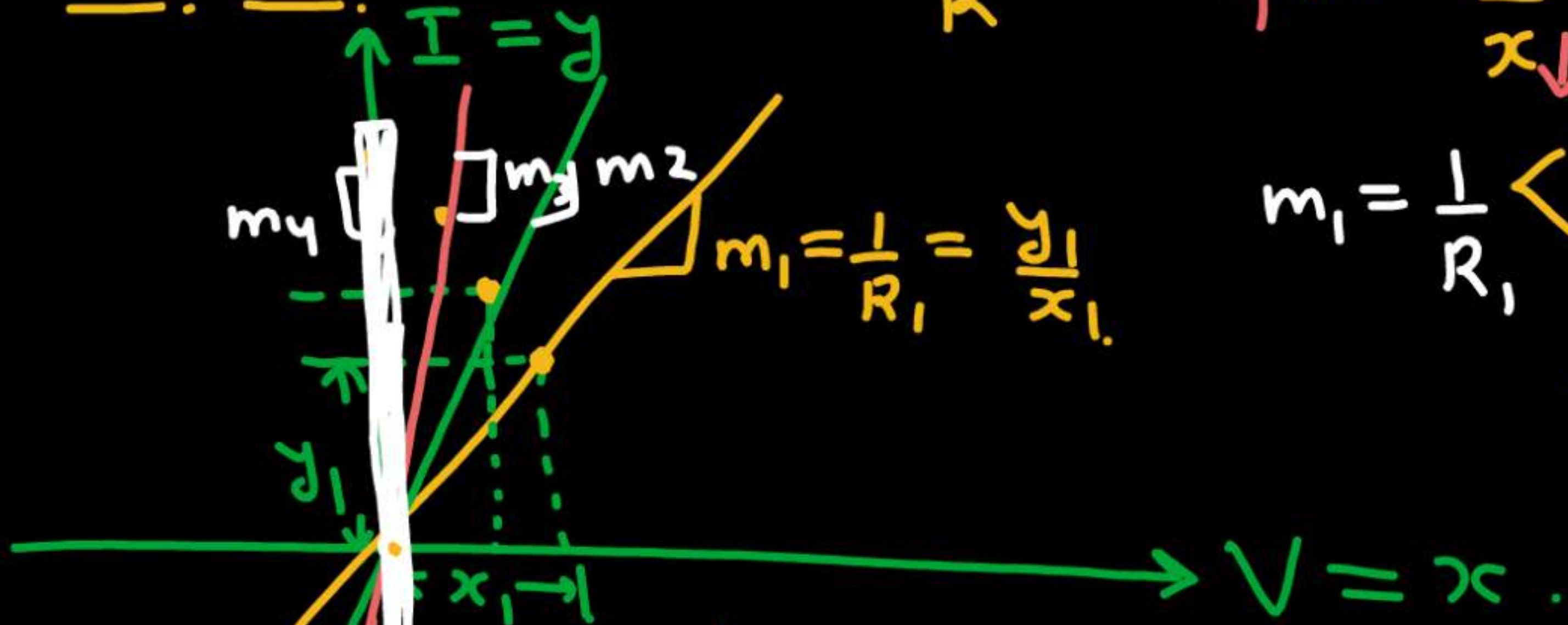[ Case-I Now  $m = \frac{1}{R} \uparrow$   $\uparrow m = \frac{y \uparrow}{x \downarrow} = \frac{1}{R \downarrow}$  ]



$$m_1 = \frac{1}{R_1} < m_2 = \frac{1}{R_2} < m_3 = \frac{1}{R_3} < m_4 = \frac{1}{R_4}$$

$$\frac{1}{R_1} < \frac{1}{R_2} < \frac{1}{R_3} < \frac{1}{R_4}$$

or

$$R_1 > R_2 > R_3 > R_4$$

• if  $R = 0, m = \infty$

$x = V = 0 \text{ V (Always)}$

$y = I = \oplus, 0, \ominus$

Short circuit ckt. Anything.

Decrease.

$R_{\min} = 0 \Omega$

$m = \frac{1}{R} = \frac{y}{x} \rightarrow \infty$   
 $R \rightarrow 0 \quad x \rightarrow 0$



[ case-II. Now decreasing the slope ( $m = \frac{1}{R} \downarrow$  ) ]

$$\downarrow m = \frac{y \downarrow}{x \uparrow} = \frac{1}{R \uparrow}$$

$$m_1 = \frac{1}{R_1} > m_2 = \frac{1}{R_2} > m_3 = \frac{1}{R_3} > m_4 = \frac{1}{R_4}$$

$$\frac{1}{R_1} > \frac{1}{R_2} > \frac{1}{R_3} > \frac{1}{R_4}$$

$$R_1 < R_2 < R_3 < R_4$$


• if  $R_{\max} \Rightarrow \infty$

$$0 \leftarrow m = \frac{1}{R \rightarrow \infty} = \frac{y}{x \rightarrow \infty}$$

$I = 0$  A (Always)


$V = \oplus, 0, \ominus = \text{Anything}$

0.5 condition.

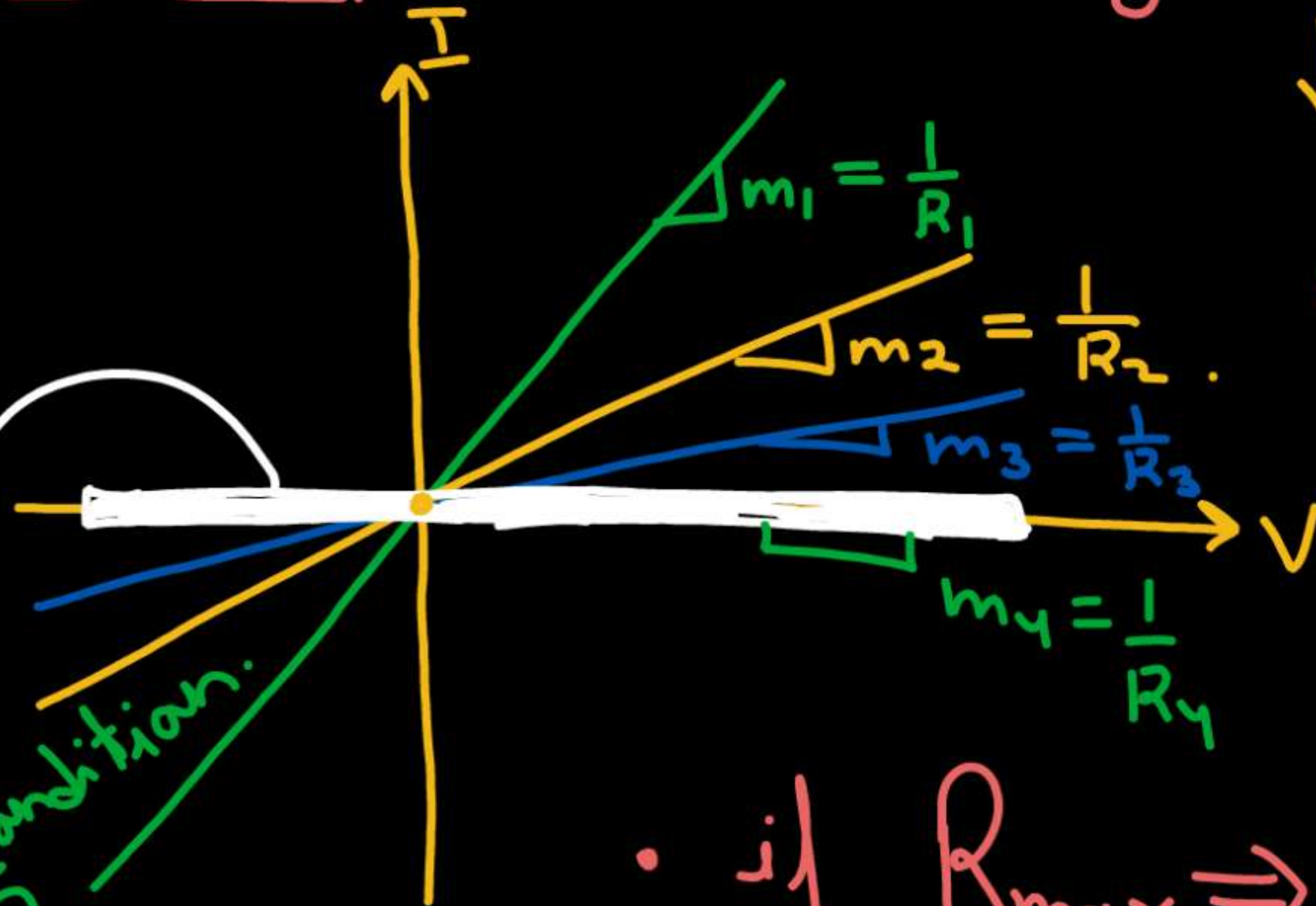



[ KVL & KCL ]

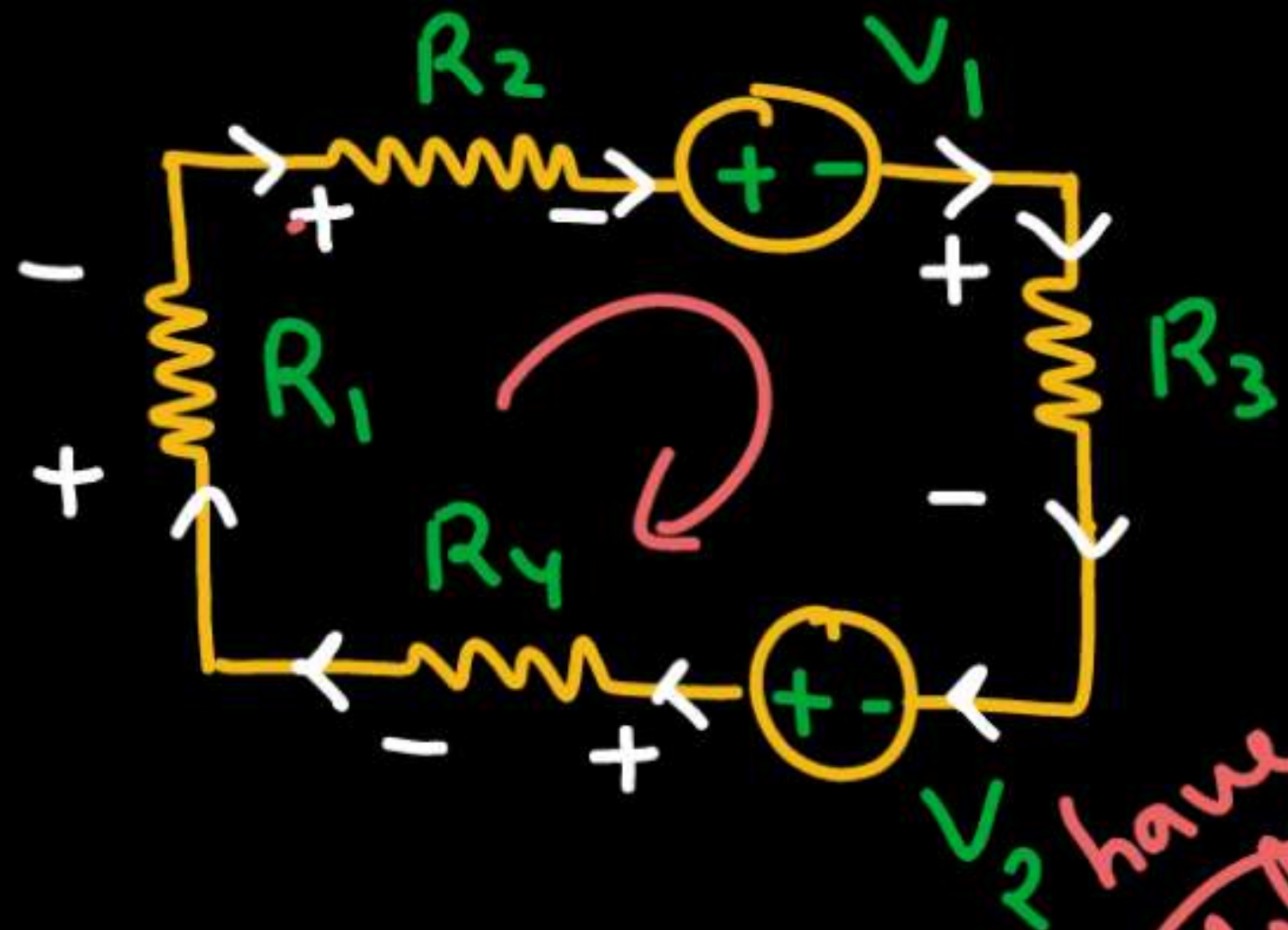



$R \rightarrow$  Always absorbs energy & dissipate it

$L \rightarrow$  It absorbs energy  $\rightarrow$  store energy

$C \rightarrow$  It absorbs energy  $\rightarrow$  store energy

• KVL  $\rightarrow$

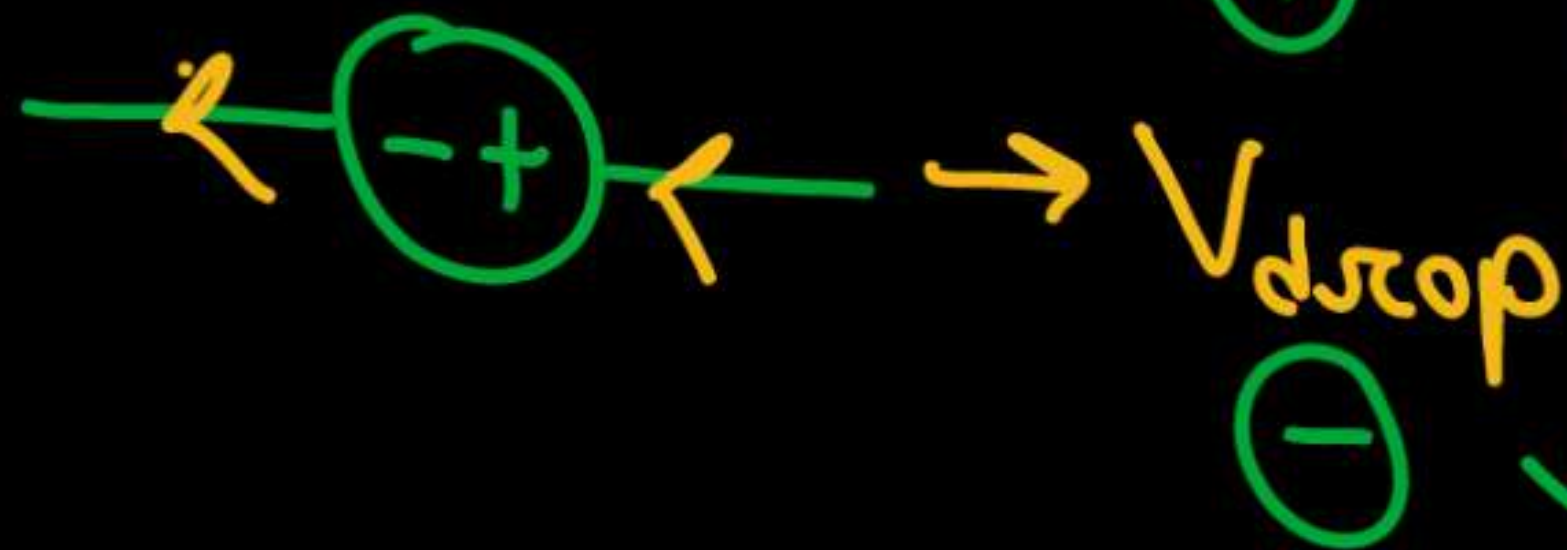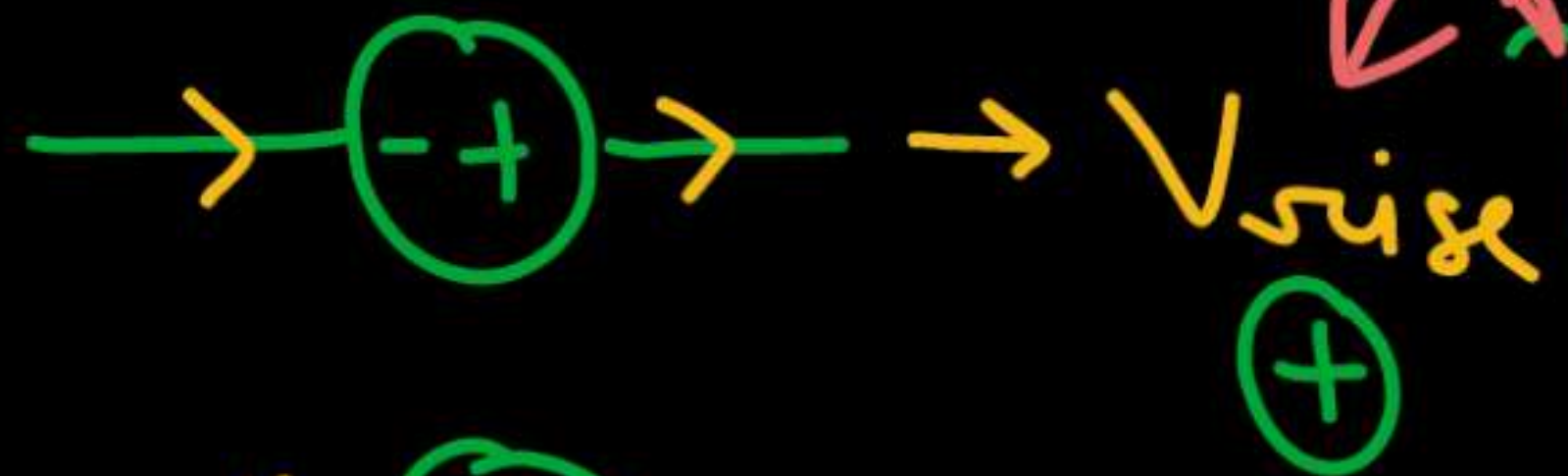we have to follow  $\left[ \sum V_{\text{loop}} = 0 \right] \rightarrow$  First Approach.



we have to follow one convention:

$$\left[ -V_{R2} - V_1 - V_{R3} + V_2 - V_{R4} - V_{R1} = 0 \right]$$



$$\left[ \begin{array}{l} \bullet -V_{R2} - V_1 + V_2 - V_{R3} - V_{R4} - V_{R1} = 0 \end{array} \right]$$

$$V_2 = V_{R1} + V_{R2} + V_{R3} + V_{R4} + V_1$$

$$\sum V_{\text{rise}} = \sum V_{\text{drop}}$$


———— 2<sup>nd</sup> approach

→ You need not to follow any convention as you have to take  $V_{\text{rise}} \& V_{\text{drop}} = \oplus$ .






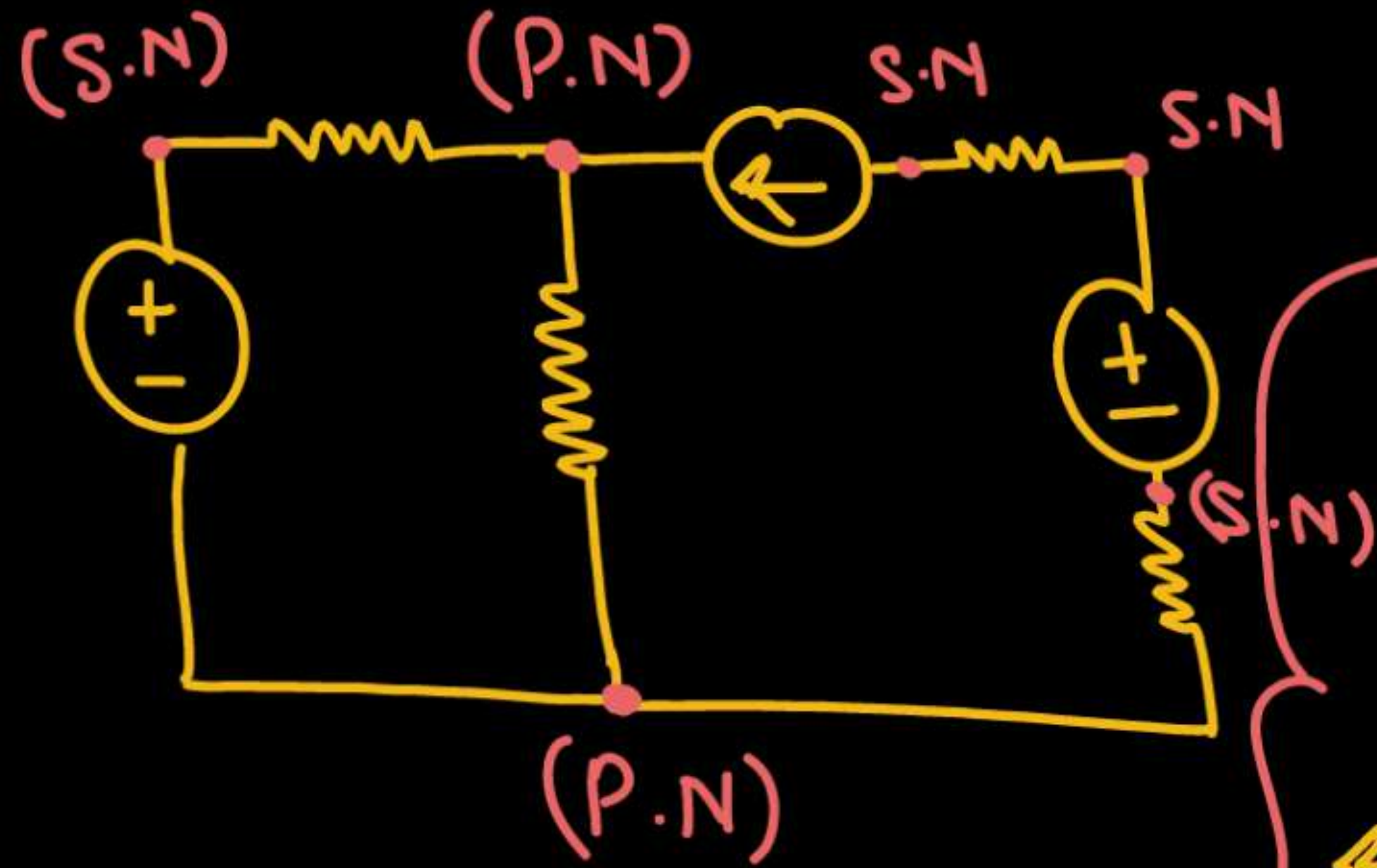[ KCL  $\rightarrow$  Applicable on Node.  
 Principle Node (P.N)  $\rightarrow$  If more than 2 element connected.  
 Simple Node (S.N)  $\rightarrow$  connection point of two elements only. ]



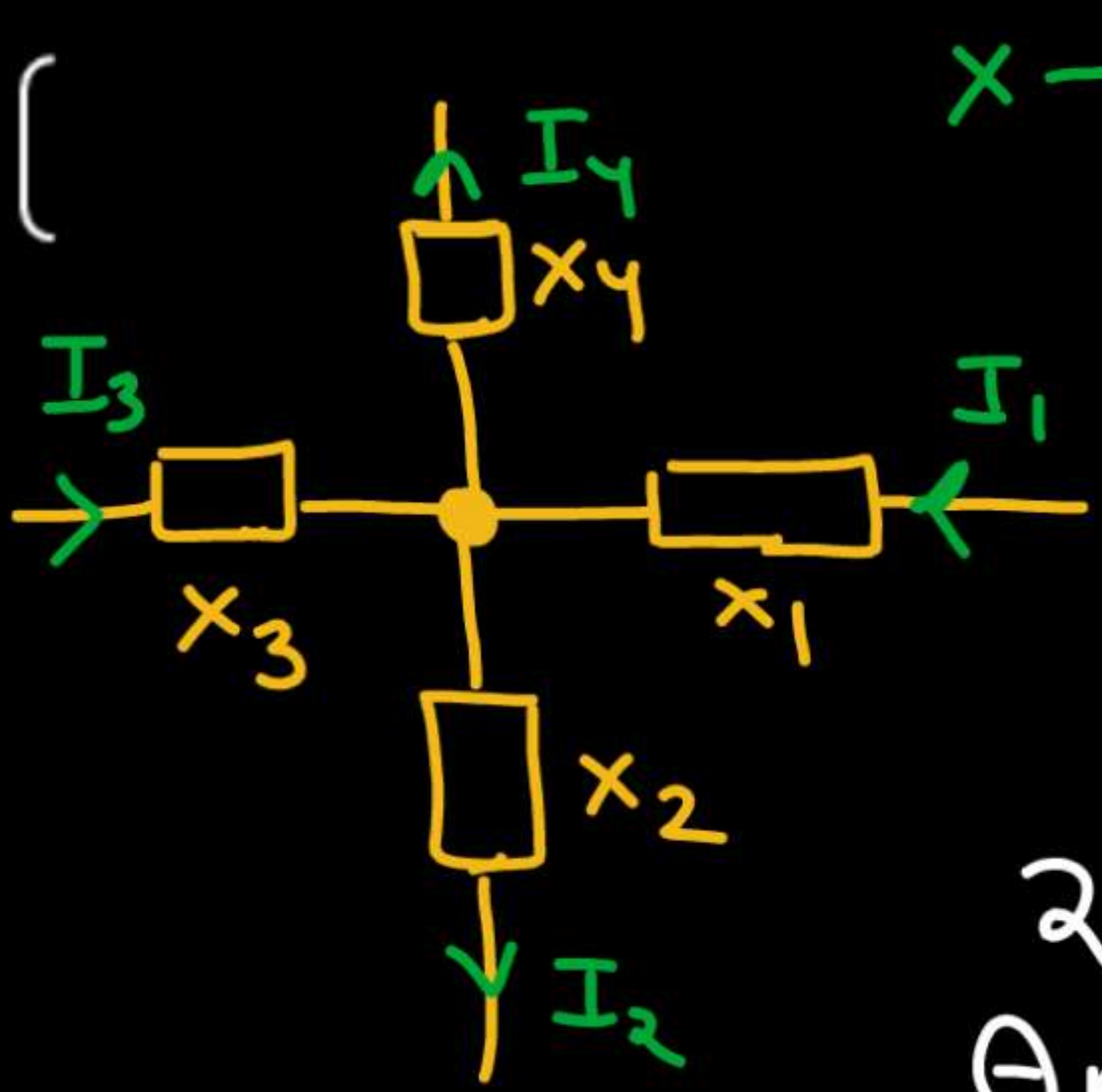$\sum I_{\text{node}} = 0$   $\rightarrow$  1<sup>st</sup> Approach  
 You need some convention  
 $\left\{ \begin{array}{l} \rightarrow \text{outgoing current} \rightarrow + \\ \rightarrow \text{Incoming current} \rightarrow - \end{array} \right.$





$x \rightarrow$  Any element

- $[-I_1 + I_4 + I_2 - I_3 = 0]$

- $I_2 + I_4 = I_1 + I_3$

2<sup>nd</sup>.  
Approach.  
(Best)

$$\sum I_{\text{outgoing}} = \sum I_{\text{incoming}}$$

$\rightarrow$  You do not need any convention.



## [ Important conclusion: ]



- KVL & KCL are Independent of Nature of Element.

- For the validity of the circuit


(1) KVL Must be Satisfied.

(2) KCL Must be Satisfied.

(3) Energy Conservation Must be Satisfied.

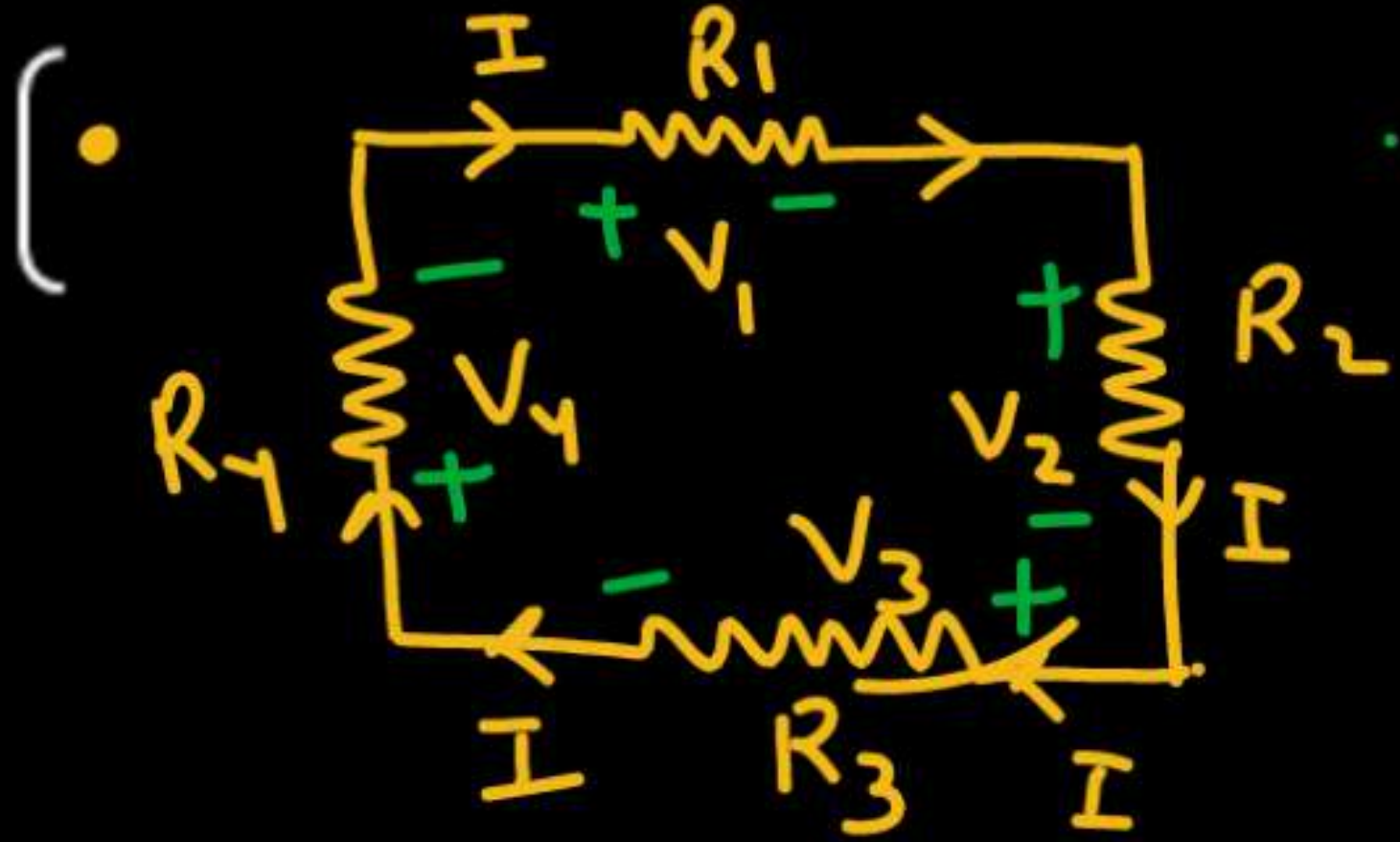(4) Charge conservation Must be Satisfied.






$$V_1 + V_2 + V_3 + V_4 = 0$$

$$\frac{d\omega_1}{d\ell} + \frac{d\omega_2}{d\ell} + \frac{d\omega_3}{d\ell} + \frac{d\omega_4}{d\ell} = 0$$

$$d\omega_1 + d\omega_2 + d\omega_3 + d\omega_4 = 0$$

→ energy conservation.

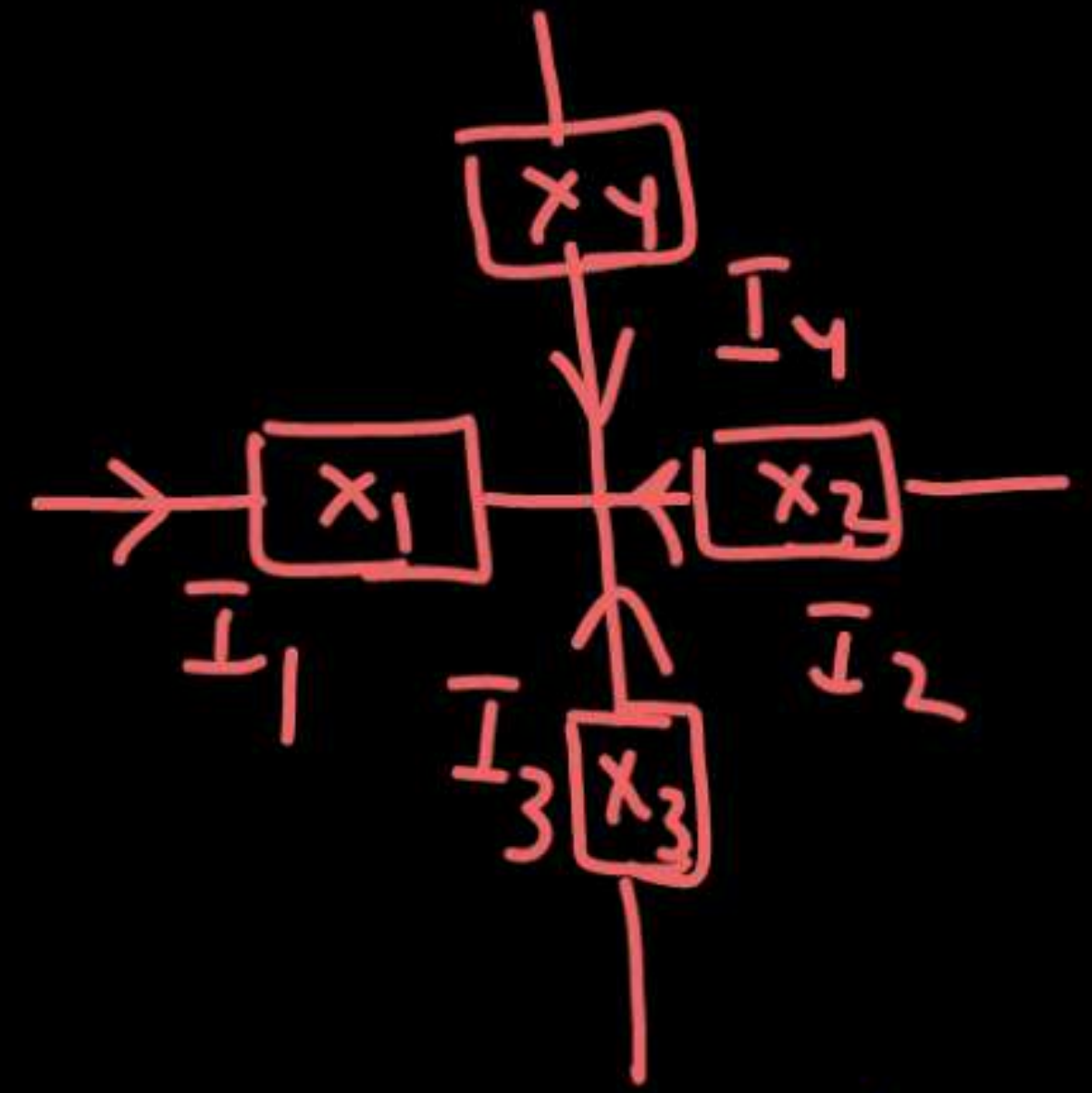


$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\frac{dq_1}{dt} + \frac{dq_2}{dt} + \frac{dq_3}{dt} + \frac{dq_4}{dt} = 0$$

Charge Conservation.  $\left[ dq_1 + dq_2 + dq_3 + dq_4 = 0 \right]$



# [ Topic-04 (Energy Sources) ]

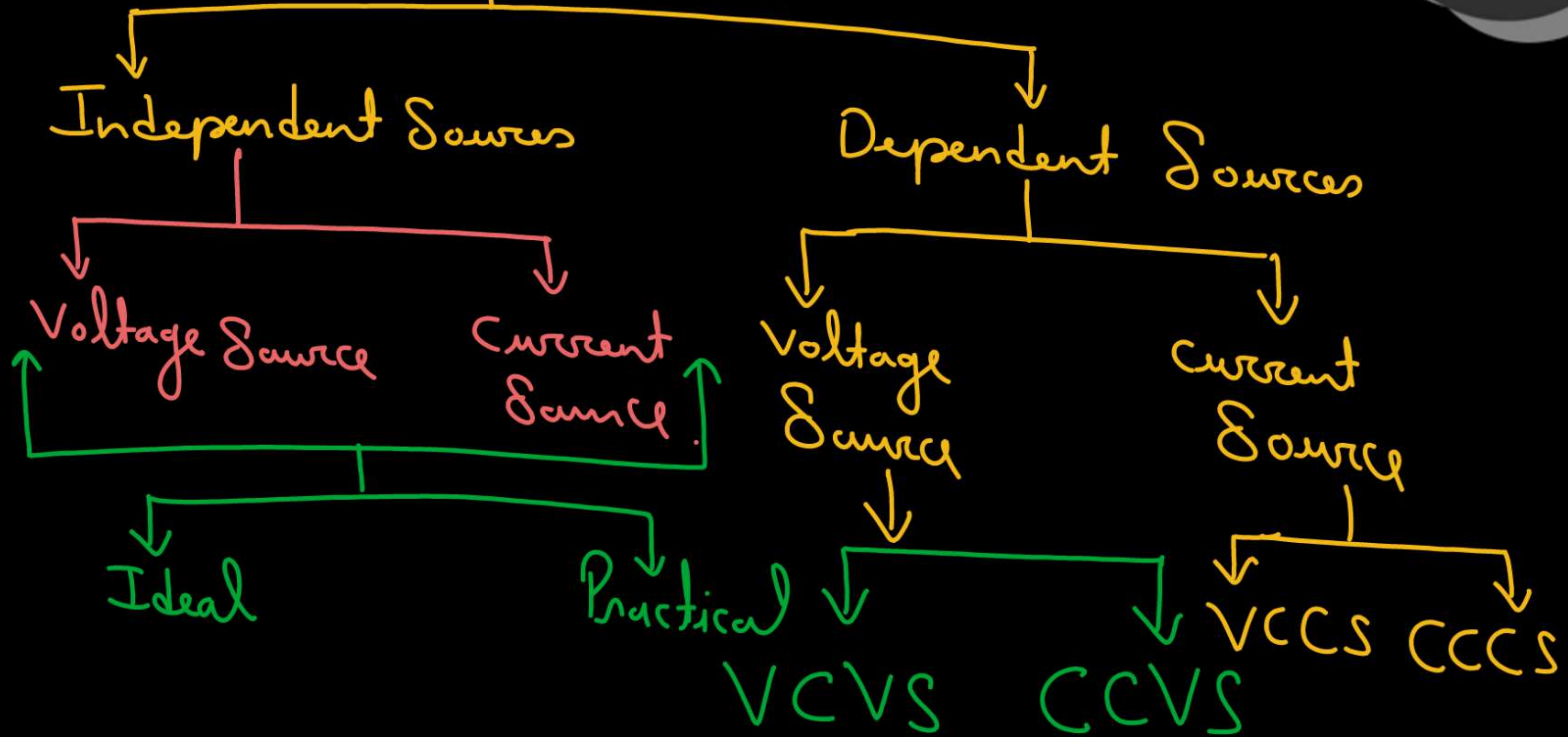



$$\left[ \begin{array}{l} \bullet \\ \sum V_{rise} = \sum V_{drop} \end{array} \right] \rightarrow \text{easy.}$$

$$\left[ V_2 = V_1 + V_{R1} + V_{R2} + V_{R3} + V_{R4} \right]$$



Thank you

**GW**  
*Soldiers !*

