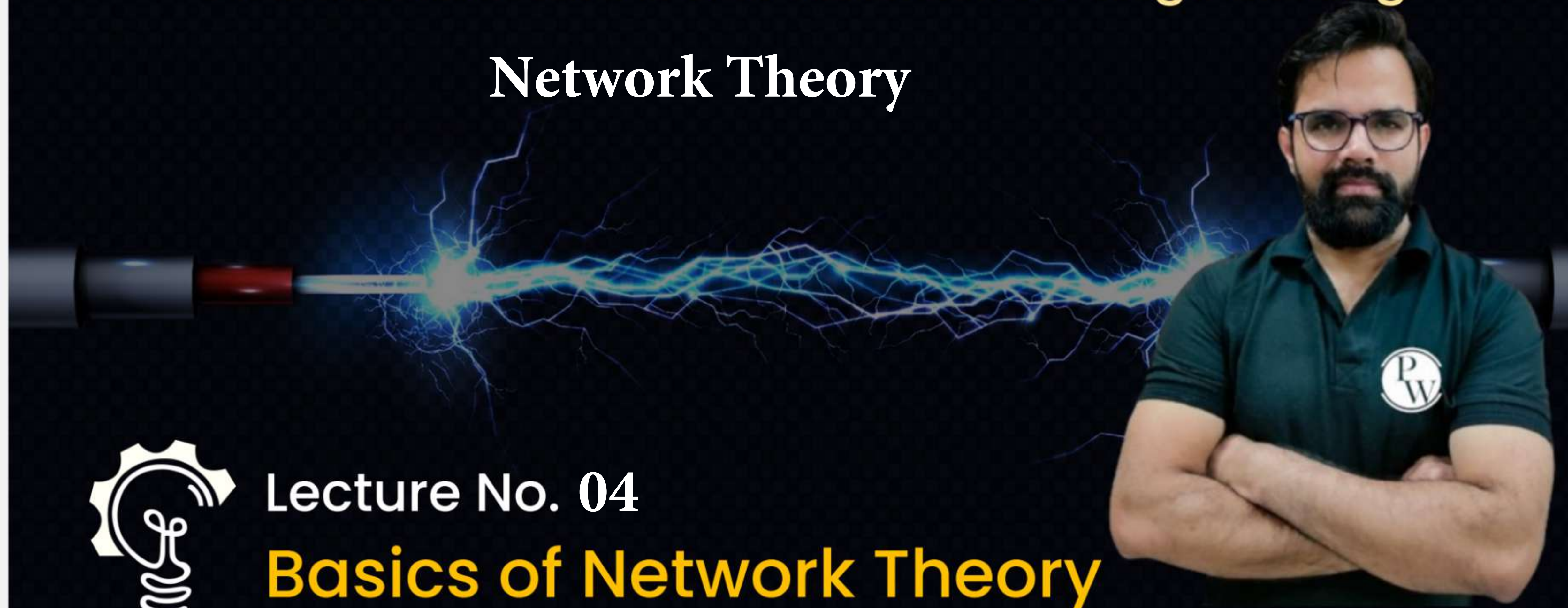


Electrical Engineering



Electronics and Communication Engineering

Network Theory



Lecture No. 04

Basics of Network Theory

By- Pankaj Shukla sir



Topics to be Covered

1. Series & Parallel operation
2. Question Discussion.
- 3.
- 4.
- 5.
- 6.

Dependent Sources: (Depending variable \rightarrow other branch voltage or current)



Voltage Source

Current Source

VCVS

CCVS

VCCS




CCCS


(Voltage controlled Voltage Source)

(Current controlled Voltage Source)

Voltage controlled Current Source

Current controlled Current Source.

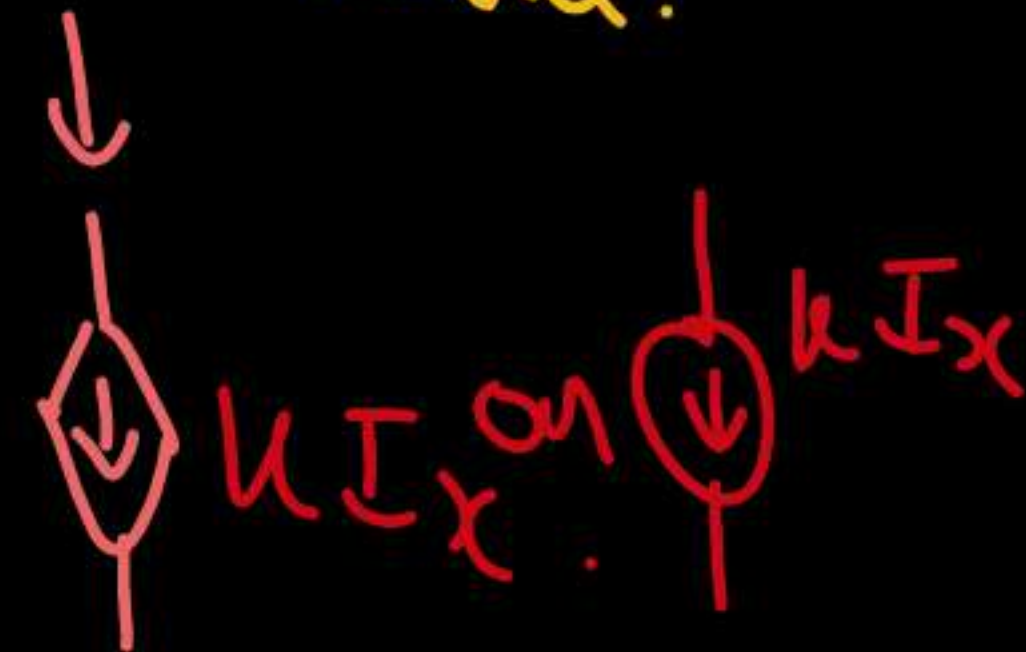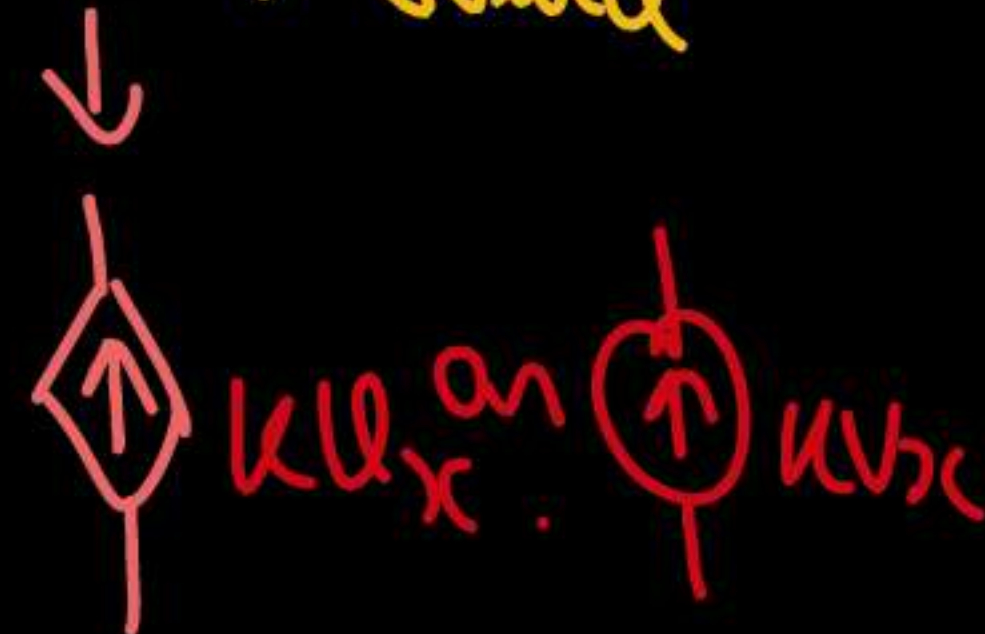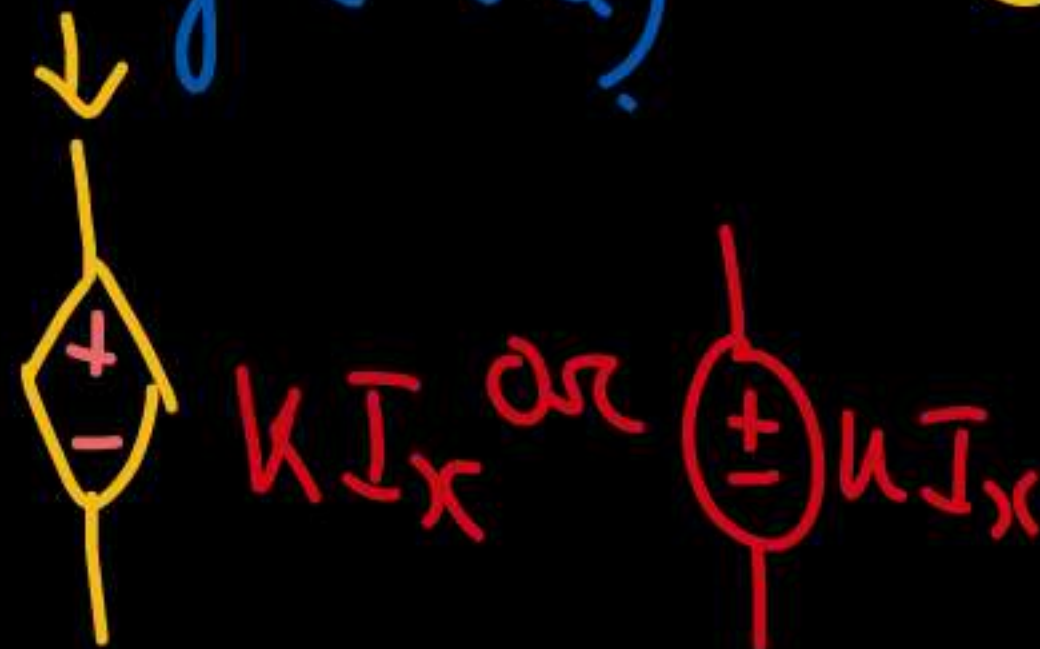

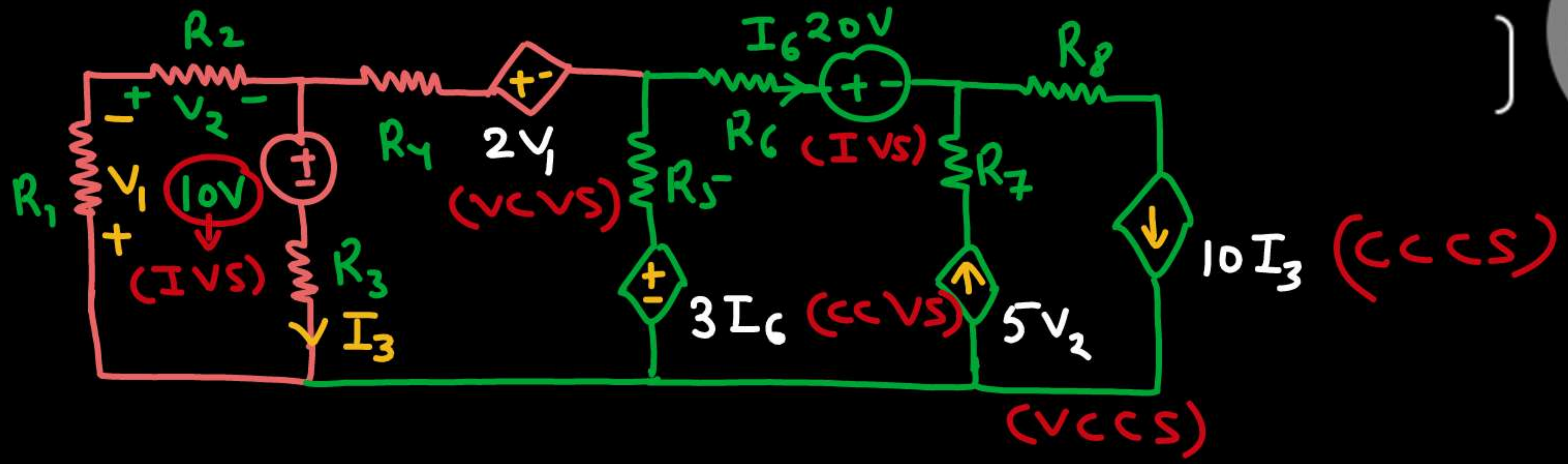


Topic - (Series & Parallel operation)

- $R \rightarrow$ Series & Parallel operation.
- current Sources \rightarrow Series & Parallel operation
- voltage Sources \rightarrow Series & Parallel operation.

Series Operation:


(+) Resistances:

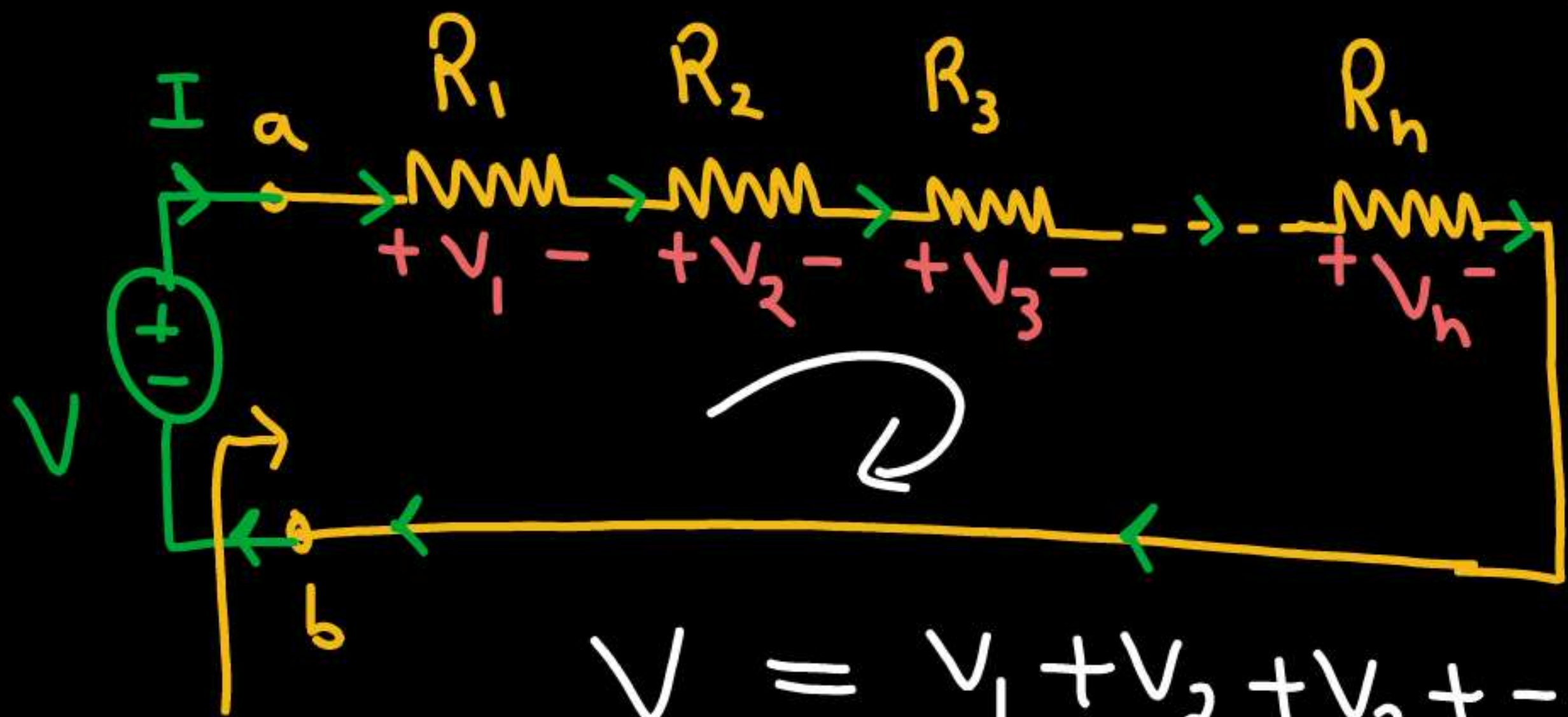- current will remain SAME (Always)
- voltage across each resistor will be different or same.



$$V = V_1 + V_2 + V_3 + \dots + V_n$$
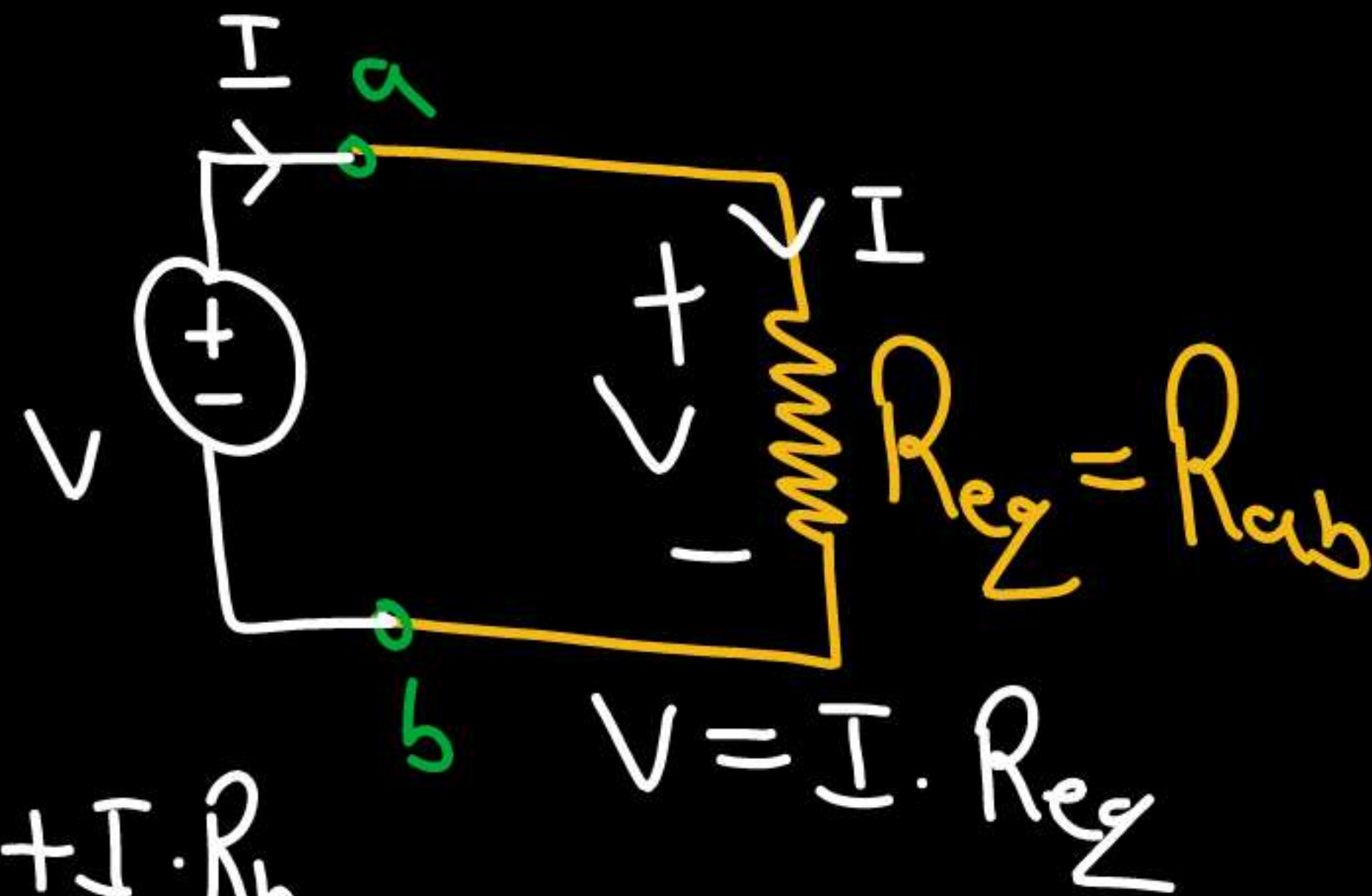
$$V = IR_1 + IR_2 + IR_3 + \dots + I \cdot R_n$$



$$\left[\begin{aligned} V &= I (R_1 + R_2 + R_3 + \dots + R_n) \\ \left[\frac{V}{I} \right] &= R_1 + R_2 + R_3 + \dots + R_n = R_{eq} = R_{ab} \end{aligned} \right] \quad \text{✓✓✓}$$

$$\begin{aligned} V_1 &= I \cdot R_1 = \left(\frac{V}{R_{eq}} \right) \times R_1 \\ V_2 &= I \cdot R_2 = \left(\frac{V}{R_{eq}} \right) \times R_2 \\ V_3 &= I \cdot R_3 = \left(\frac{V}{R_{eq}} \right) \times R_3 \\ &\vdots \\ V_n &= I \cdot R_n = \left(\frac{V}{R_{eq}} \right) \times R_n \end{aligned}$$

Hence, the General expression to find the voltage across any Resistor connected in Series.

$$V_x = V \times \left(\frac{R_x}{R_{eq}} \right) \rightarrow (V \text{ D } R)$$

$x = 1, 2, 3, \dots, n$

[• Now let's have Similar Resistance,
[$R_1 = R_2 = R_3 = \dots = R_n = R$]

(1) [$R_{eq} = R + R + R + R + \dots + R = n \cdot R$]


(2) $V_x = V \cdot \frac{R_x}{R_{eq}} = V \cdot \frac{R}{n \cdot R} = \frac{V}{n}$

[$V_R = \frac{V}{n}$] \rightarrow [$V_1 = V_2 = V_3 = \dots = V_n = \frac{V}{n}$]

(2) Voltage Sources:

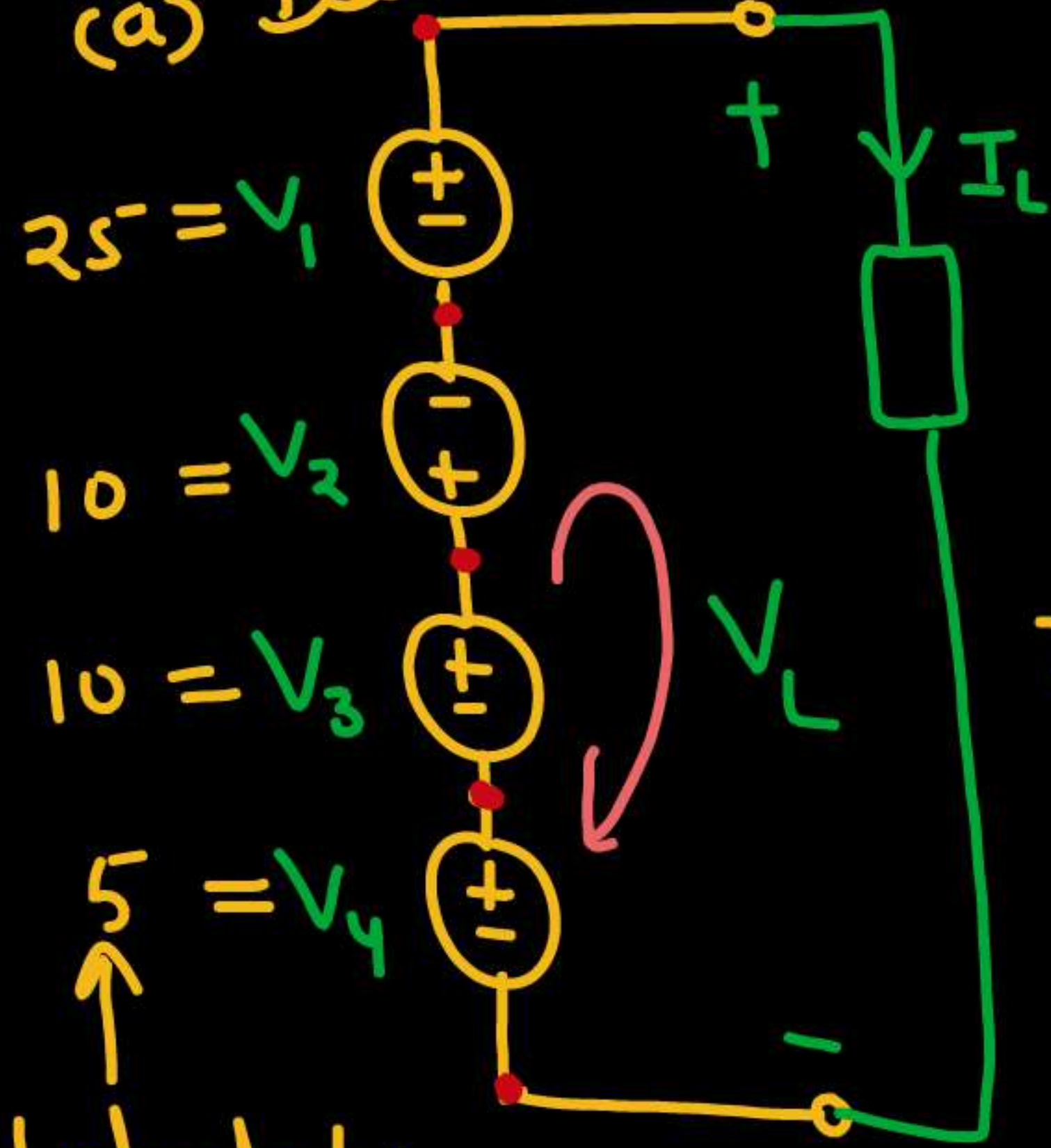(a) Ideal Voltage Source

• whenever voltage sources are connected in series, then just apply the KVL.




Let's take values.

$$V_1 + V_3 + V_4 = V_2 + V_L$$



$$[V_L = V_1 + V_3 + V_4 - V_2]$$

$$V_L = 25 + 10 + 5 - 10 = 30V$$

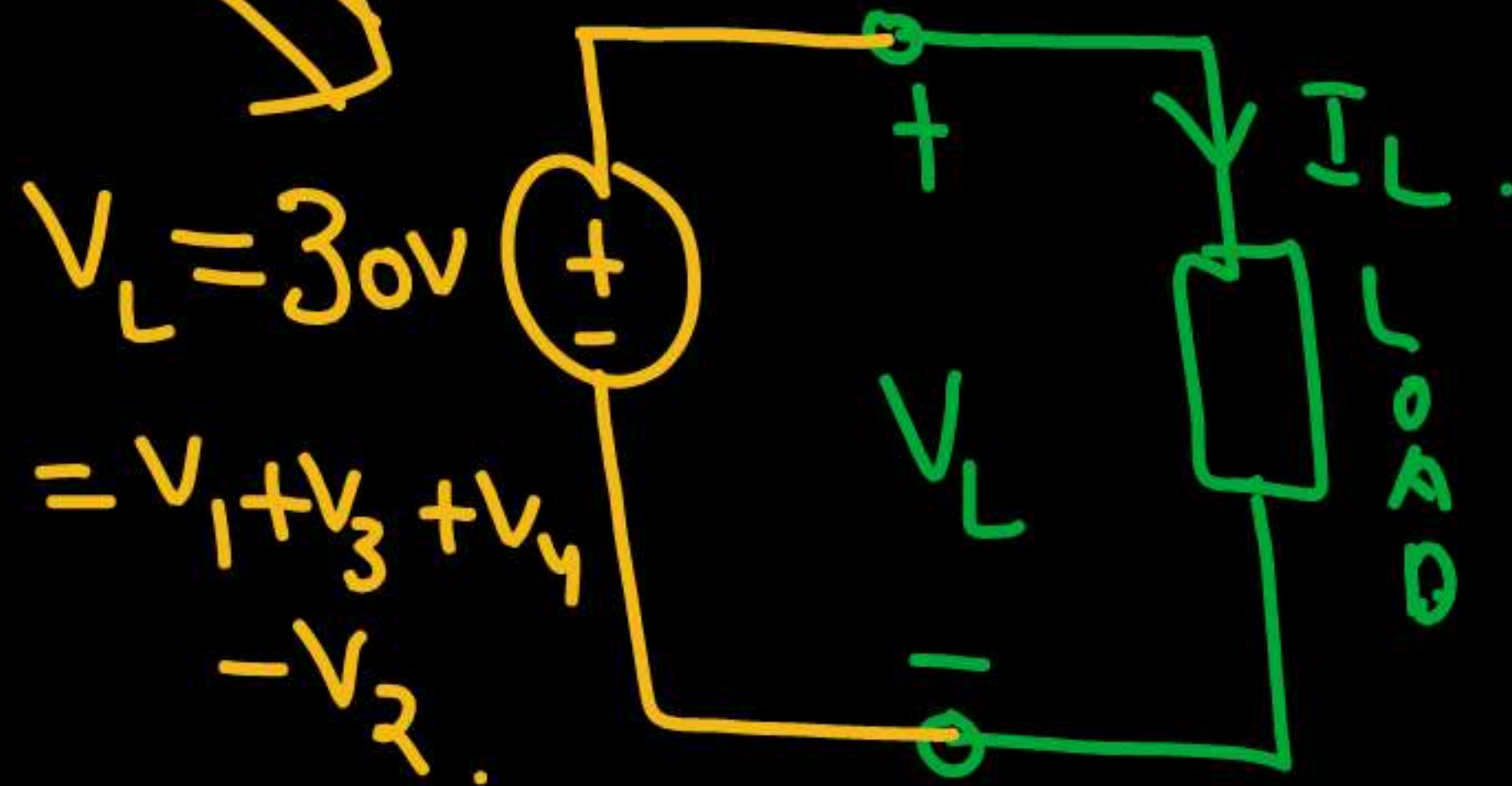


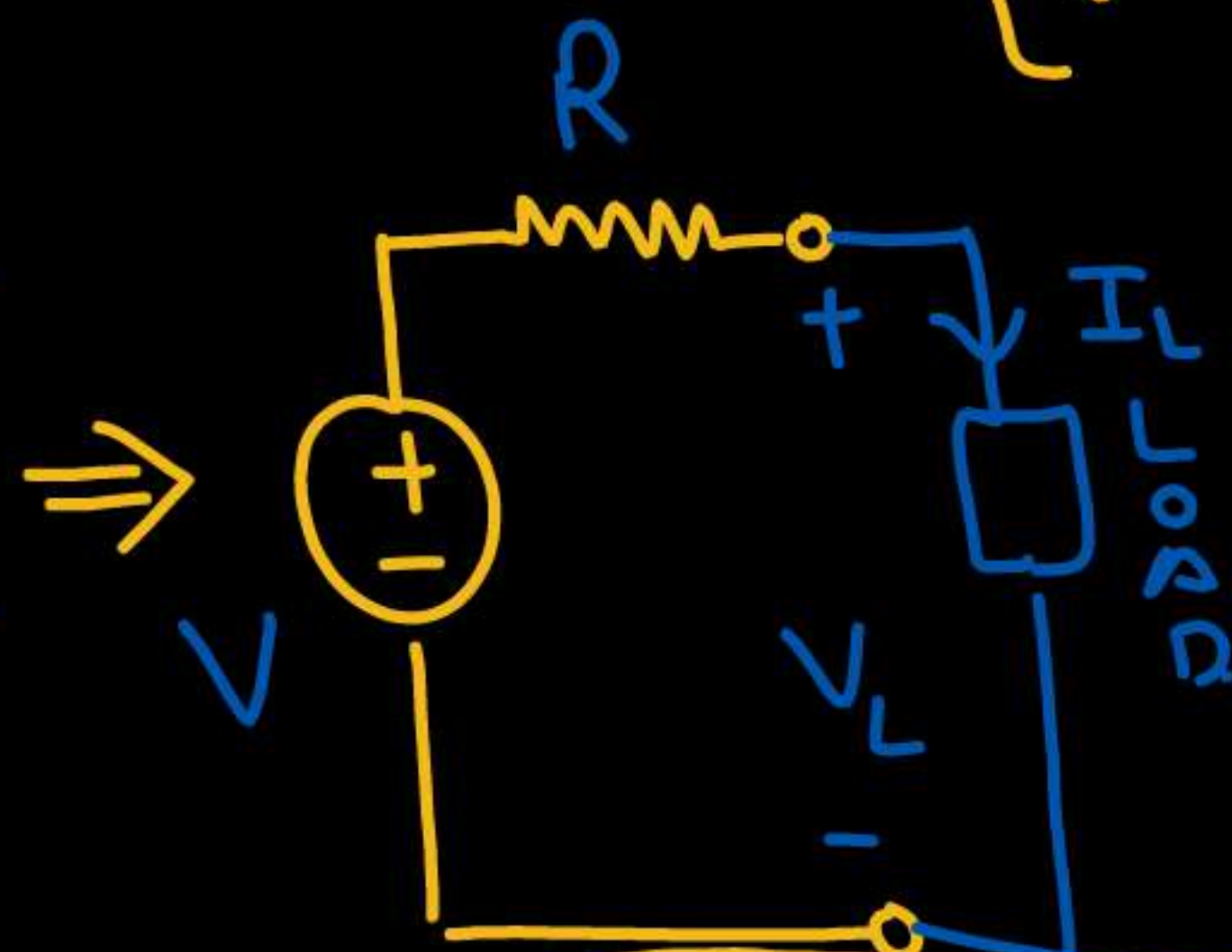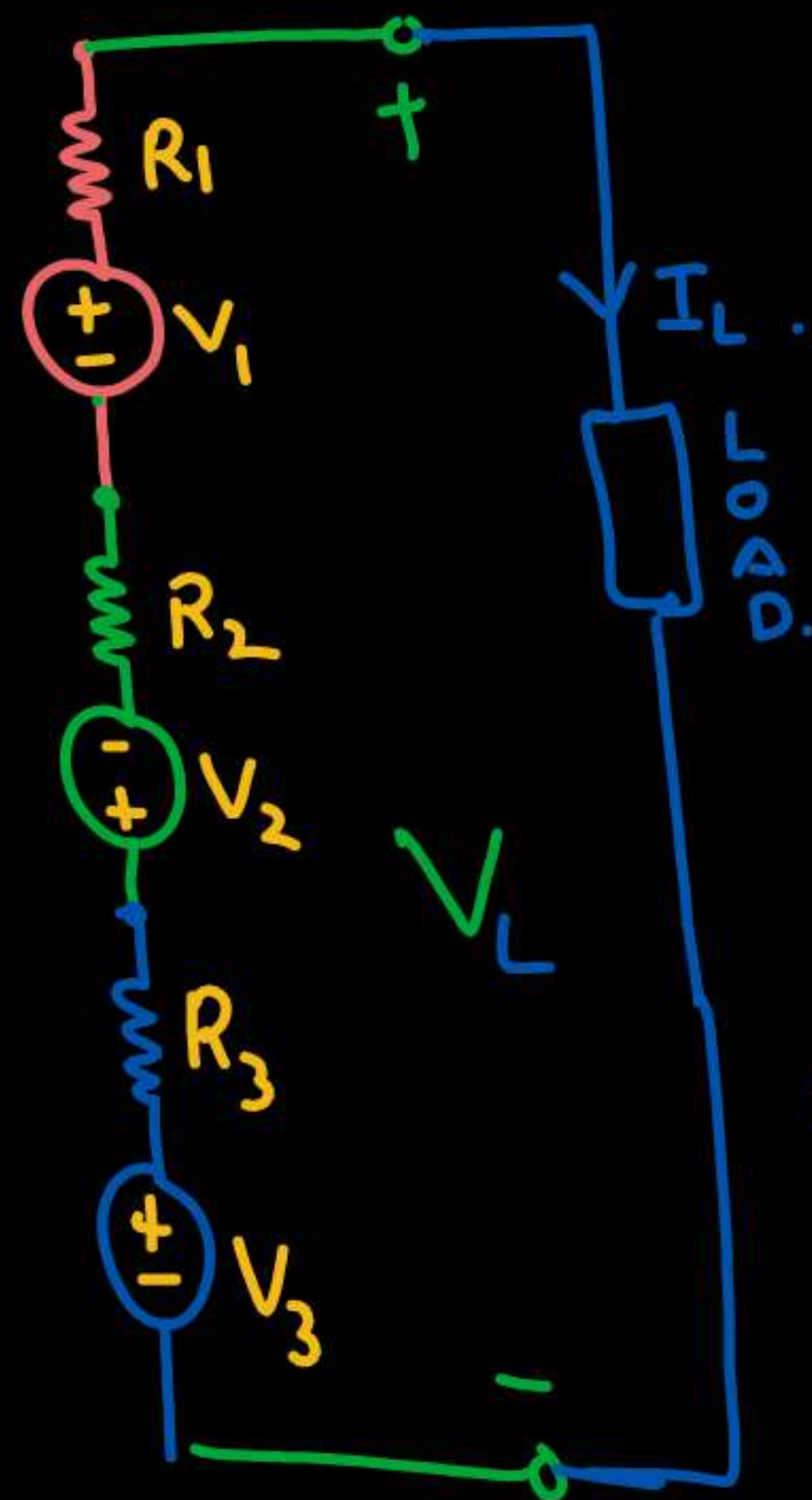(b) Practical voltage sources.



$$V + V_2 = V_1 + V_3$$
$$[V = V_1 + V_3 - V_2]$$



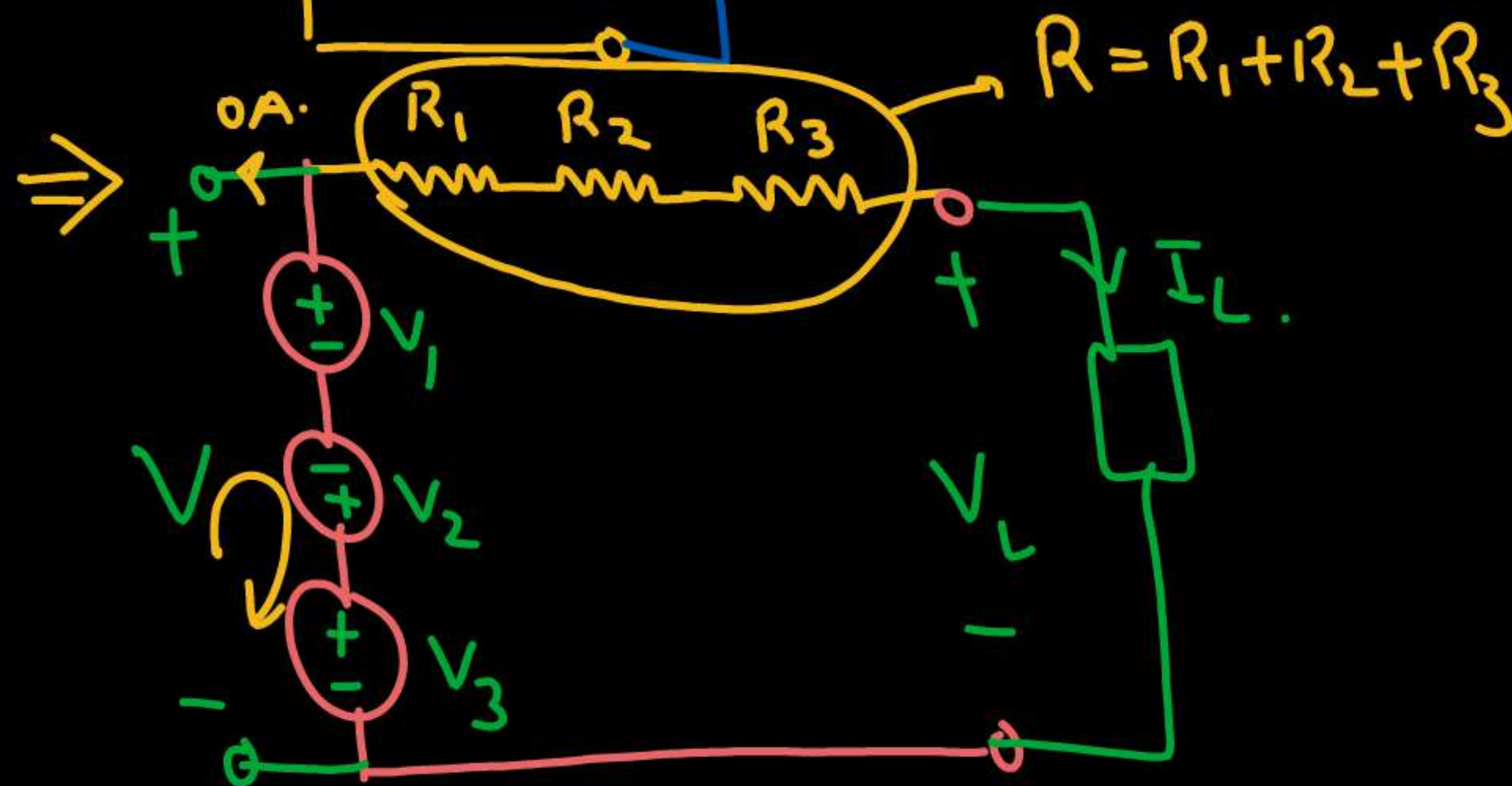→ Hence
$$\begin{cases} V = V_1 + V_3 - V_2 \\ R = R_1 + R_2 + R_3 \end{cases}$$




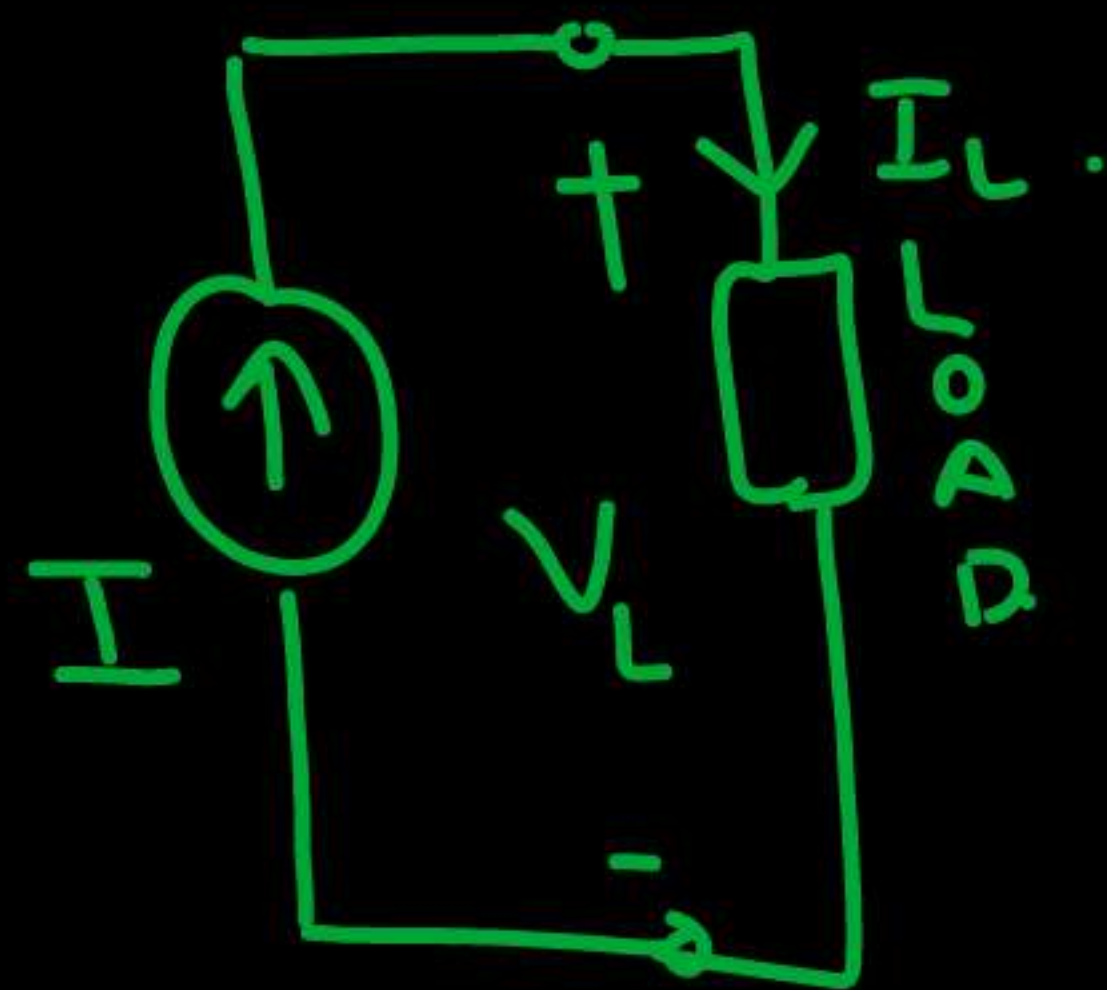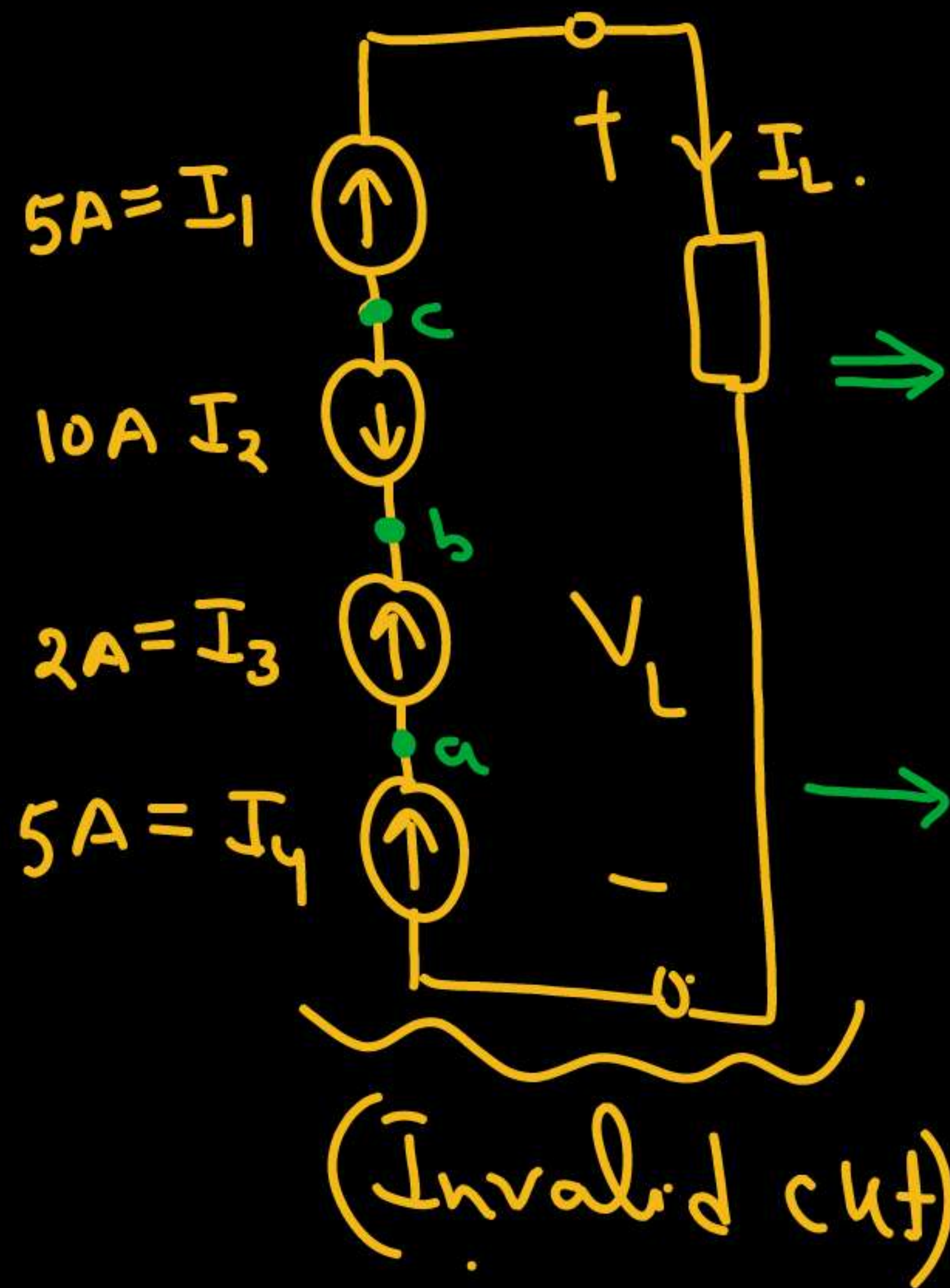③ Current Sources: (Always apply KCL & it must satisfy)



operation is not possible as KCL → fail.

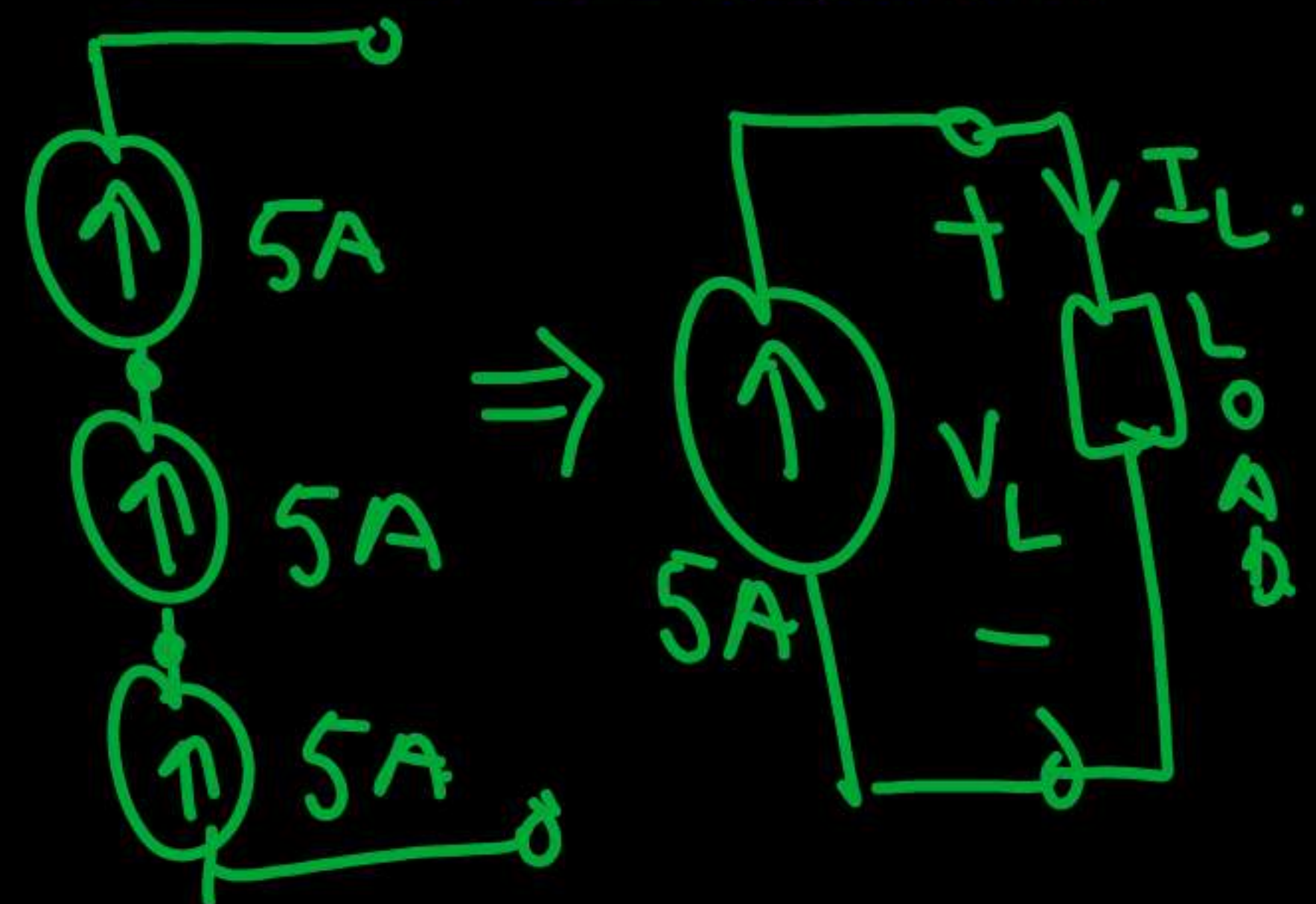- Now the Series operation of current Sources is only possible if All the currents are same value & Same direction.





[Note: if Practical current Sources are connected in series
then how to Proceed \rightarrow we will see later.]



Parallel operation:

(1) Resistors

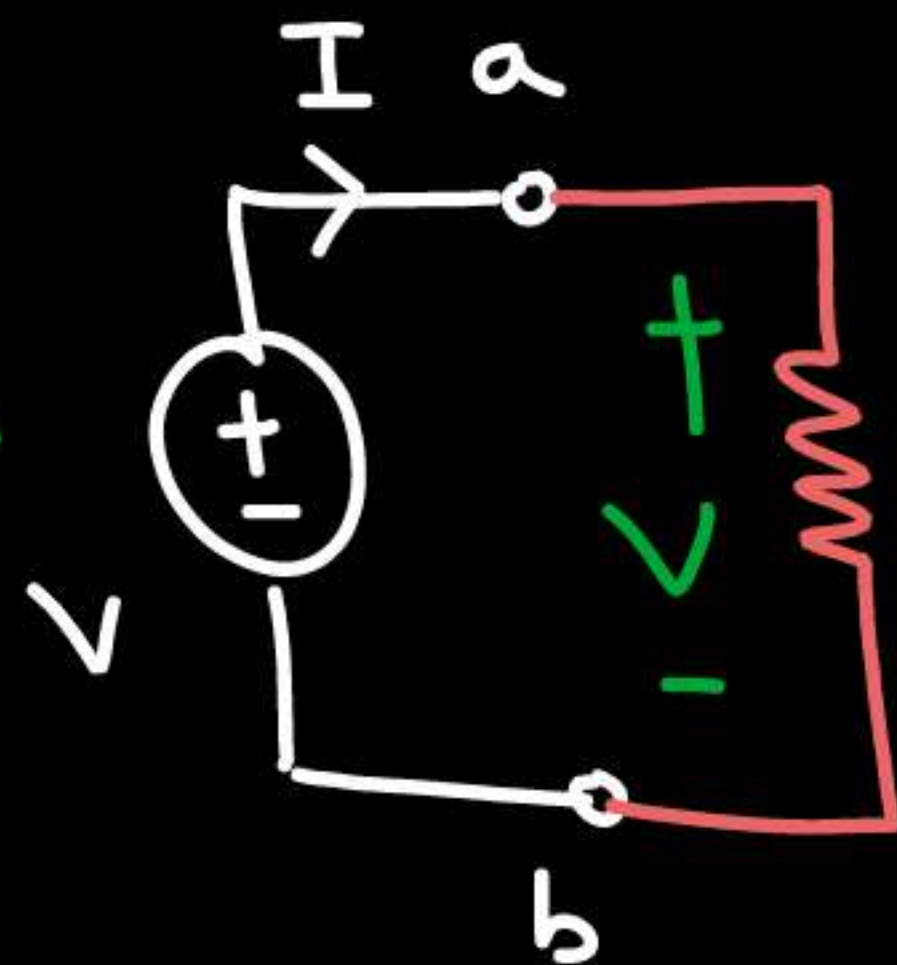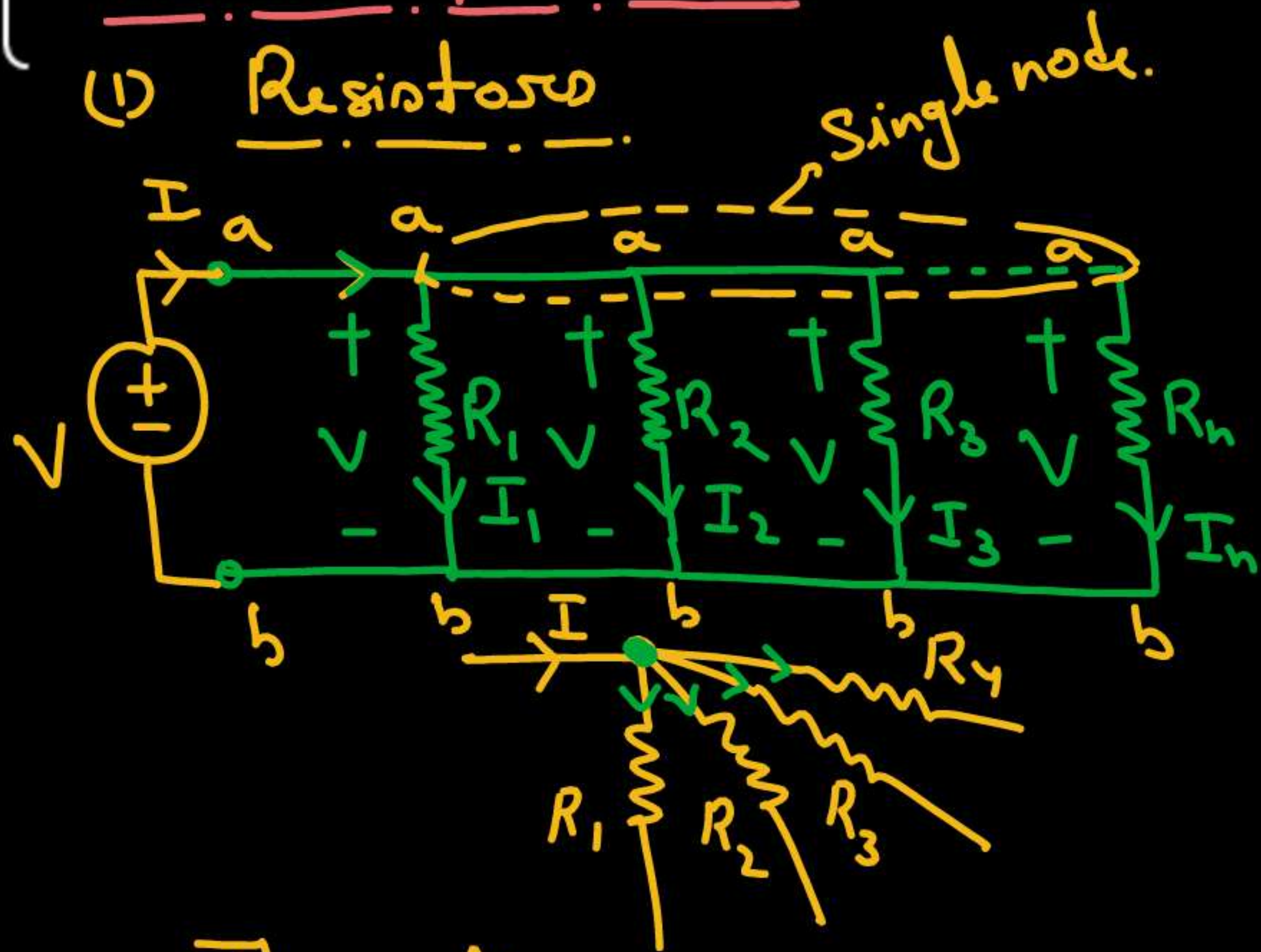

$$V = I \cdot R_{eq}$$
$$\frac{I}{V} = \frac{1}{R_{eq}}$$

- The voltage will remain same (Always)
- The current in each Resistor will be different or same.

$$I = I_1 + I_2 + I_3 + \dots + I_n$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \dots + \frac{V}{R_n}$$

$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} \right)$$

$$\frac{I}{V} = \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

Equivalent Conductance $\rightarrow G_{eq} = G_1 + G_2 + G_3 + \dots + G_n$

- [• Now current in each Resistor.]

$$I_1 = \frac{V}{R_1} = \frac{I \cdot R_{eq}}{R_1} = \frac{I}{G_{eq}} \cdot G_1$$

$$I_2 = \frac{V}{R_2} = \frac{I}{G_{eq}} \cdot G_2$$

$$I_3 = \frac{V}{R_3} = \frac{I}{G_{eq}} \cdot G_3$$

⋮


$$I_n = \frac{V}{R_n} = \frac{I}{G_{eq}} \times G_n$$

- Hence current in each Resistor can be easily calculated by using CDR.

$$I_x = I \cdot \left(\frac{G_x}{G_{eq}} \right)$$

$x = 1, 2, 3, \dots, n.$

 → CDR

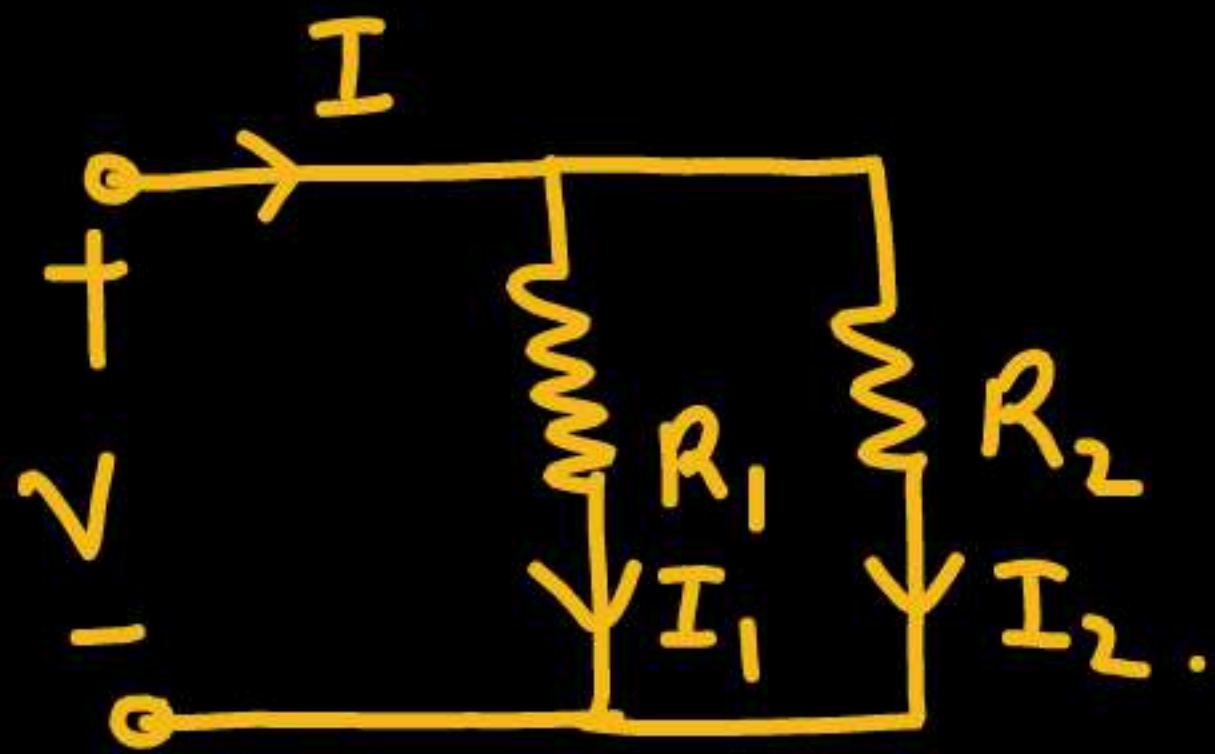

$$G_{eq} = G_1 + G_2$$

$$\frac{1}{R_{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\left[I_x = I \times \frac{G_x}{G_{eq}} \right]$$

$$I_1 = I \times \frac{G_1}{G_{eq}} = \frac{I \times \frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{I/R_1}{\left(\frac{R_1 + R_2}{R_1 R_2} \right)}$$

$$I_1 = I \times \left(\frac{R_2}{R_1 + R_2} \right)$$

$$I_2 = I \times \frac{G_2}{G_{eq}} = \frac{I \times \frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$I_2 = I \times \left(\frac{R_1}{R_1 + R_2} \right)$$

[• Now if all Resistors are same.]

$$R_1 = R_2 = R_3 = R_4 = \dots = R_n = R.$$

$$G_1 = G_2 = G_3 = G_4 = \dots = G_n = \frac{1}{R} = G$$

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R} = \frac{n}{R} \rightarrow G_{eq} = \underbrace{G + G + G + \dots + G}_{= n \cdot G}$$

$$\left[G_{eq} = \frac{1}{R_{eq}} = \frac{n}{R} \right] \text{ or } \left[R_{eq} = \frac{R}{n} \right]$$


$$\left[I_x = I \cdot \frac{G_x}{G_{eq}} = I \times \frac{G}{G_{eq}} = I \times \frac{\cancel{G}}{n \cdot \cancel{G}} = \frac{I}{n} \right]$$






② Voltage Sources:


(a) Ideal (KVL must be satisfied)

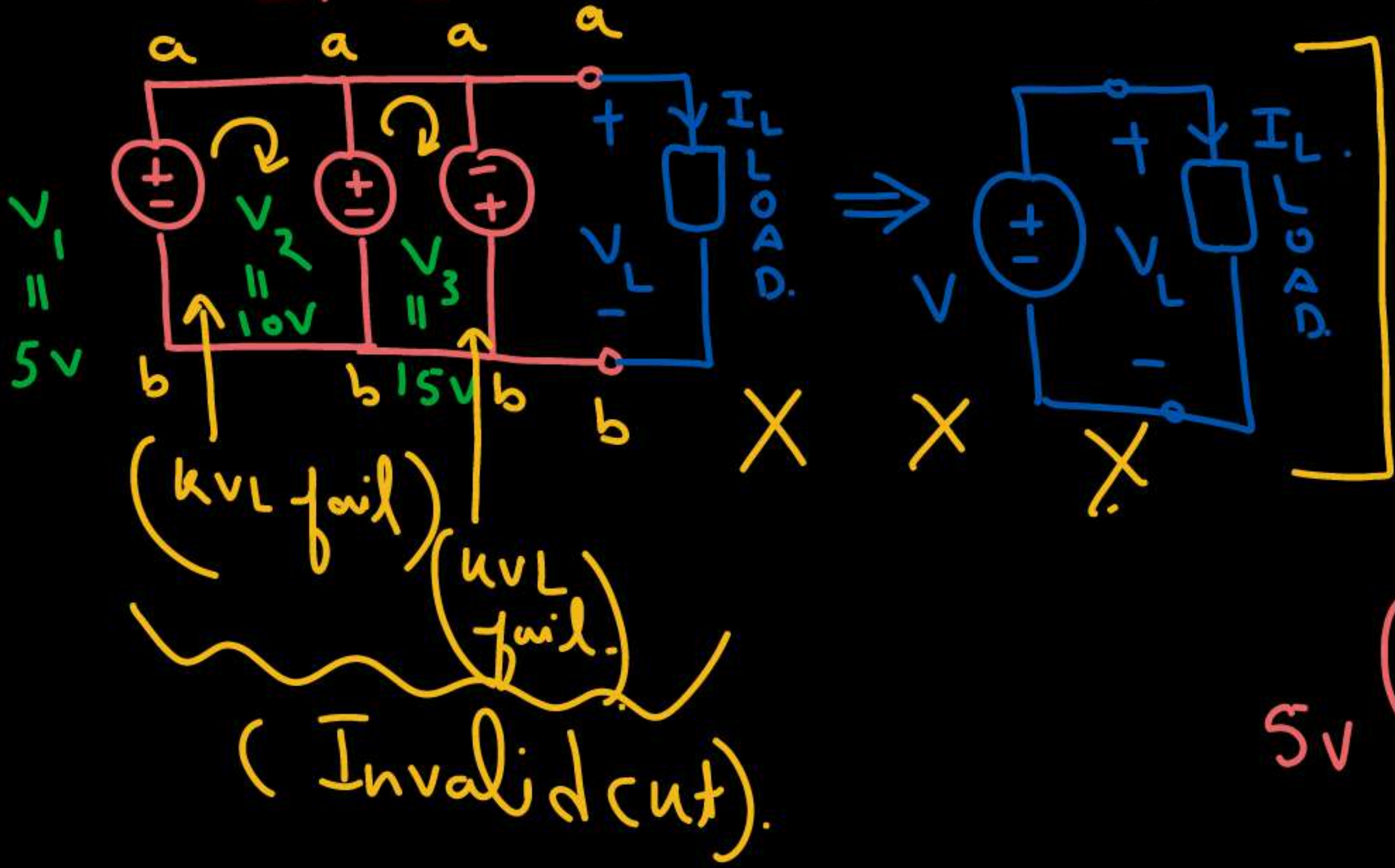

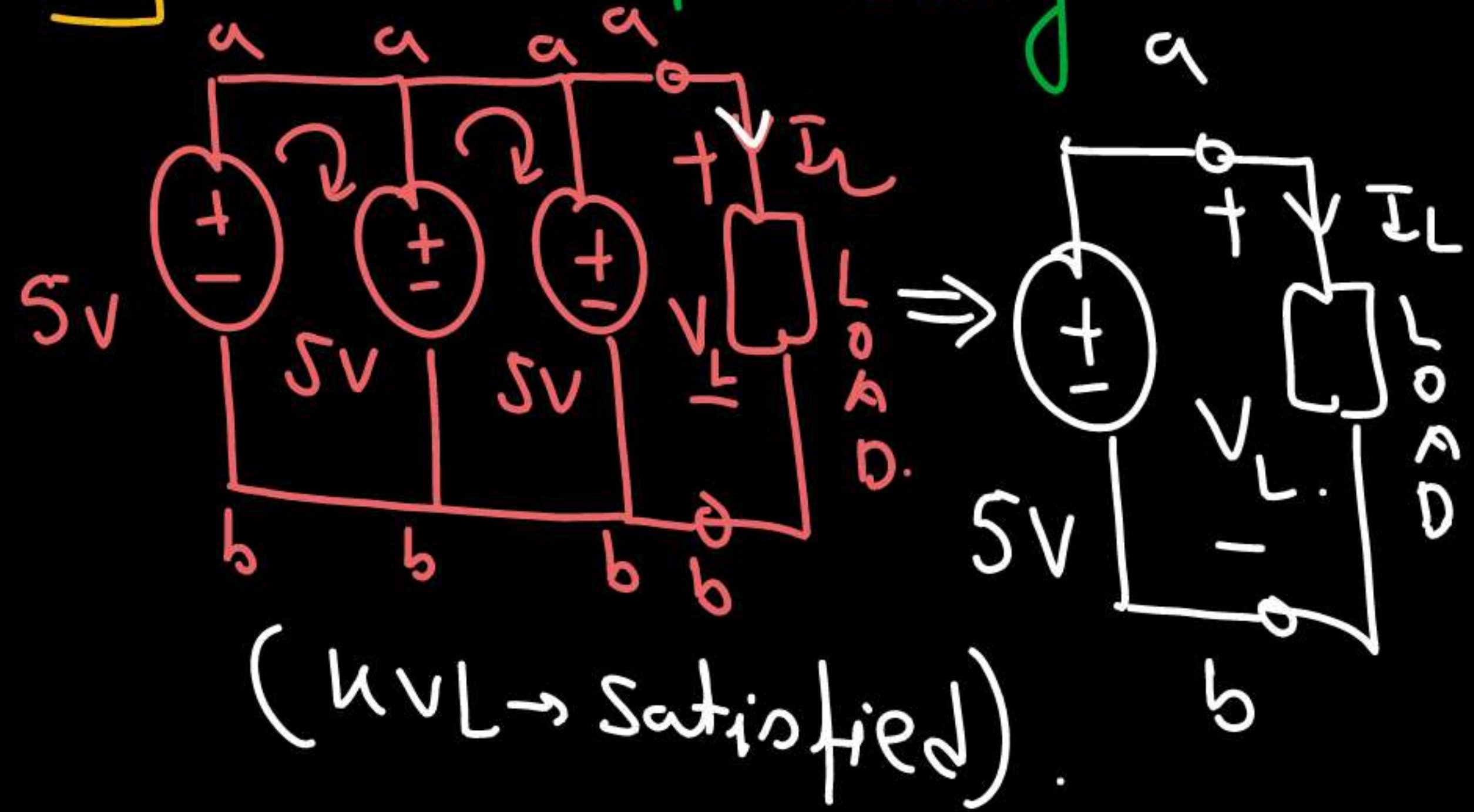Note: From the Discussion
The ideal voltage sources
can be connected in
Parallel if they have
Same Magnitude &
Same polarity.




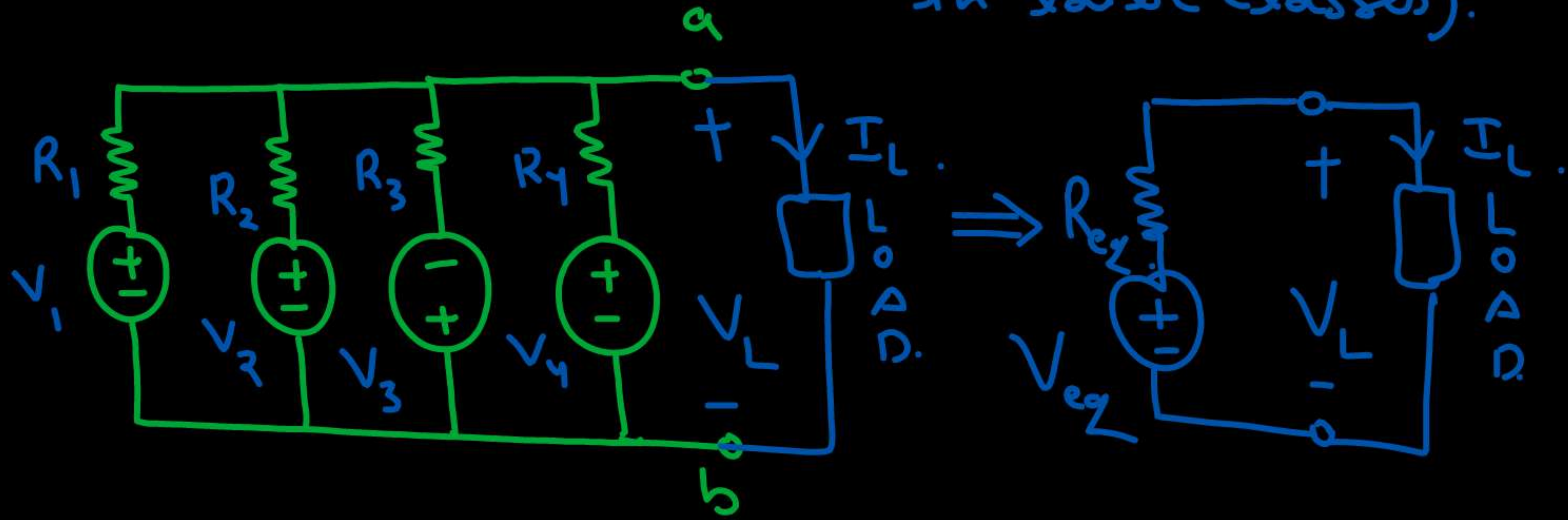(b) Practical voltage sources. (We will see this operation in later classes).



③ Current Sources.


(a) Ideal (just Apply KCL).

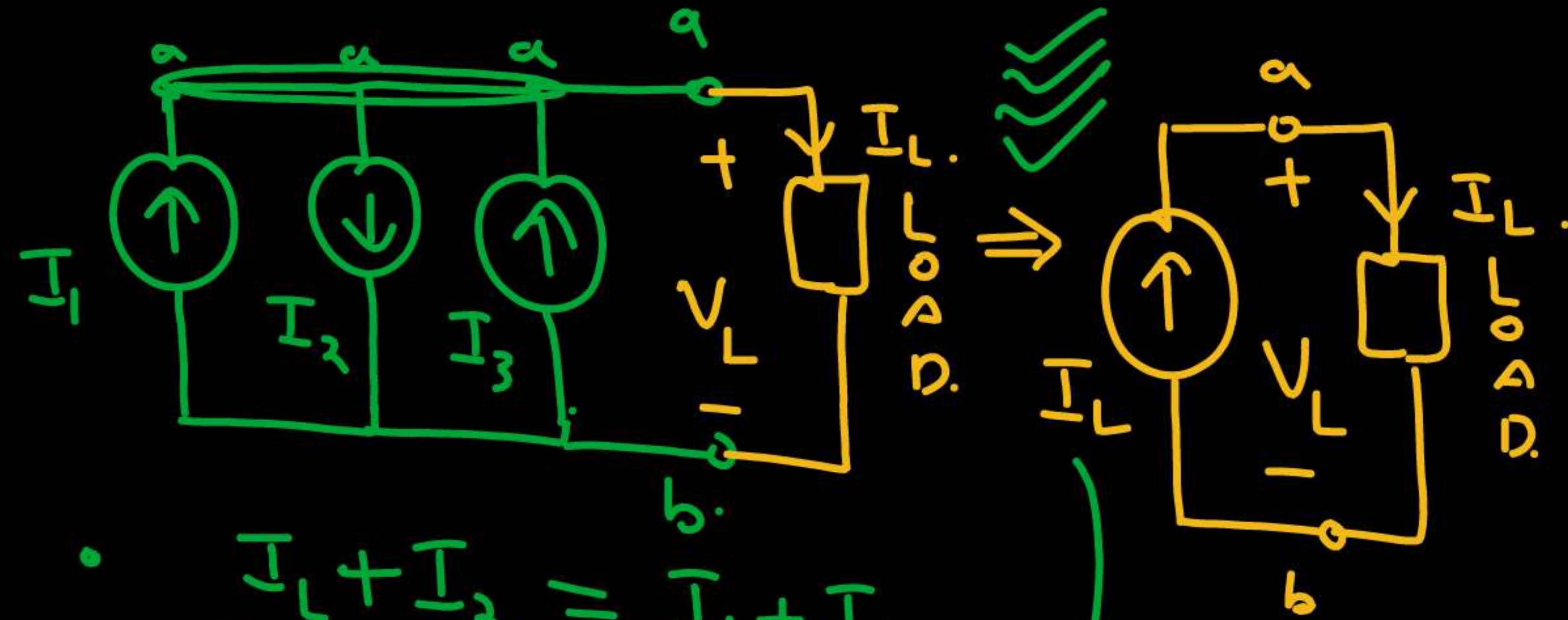

$$\begin{aligned} I_L + I_2 &= I_1 + I_3 \\ \left[I_L = I_1 + I_3 - I_2 \right] \end{aligned}$$


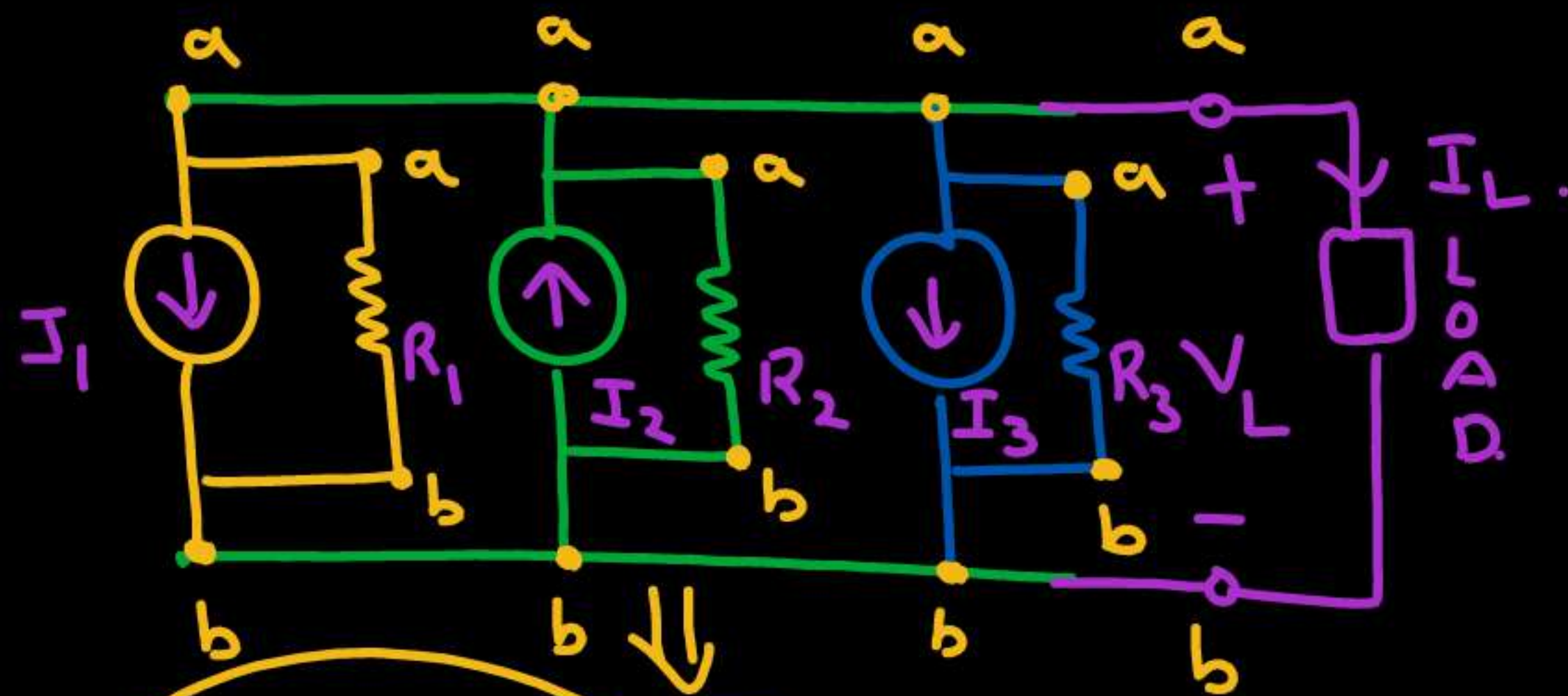
(b) Practical current sources.

$$\begin{aligned} I_1 + I_3 + I &= I_2 \\ I &= I_2 - I_1 - I_3 \end{aligned}$$



$$\left[R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right]$$
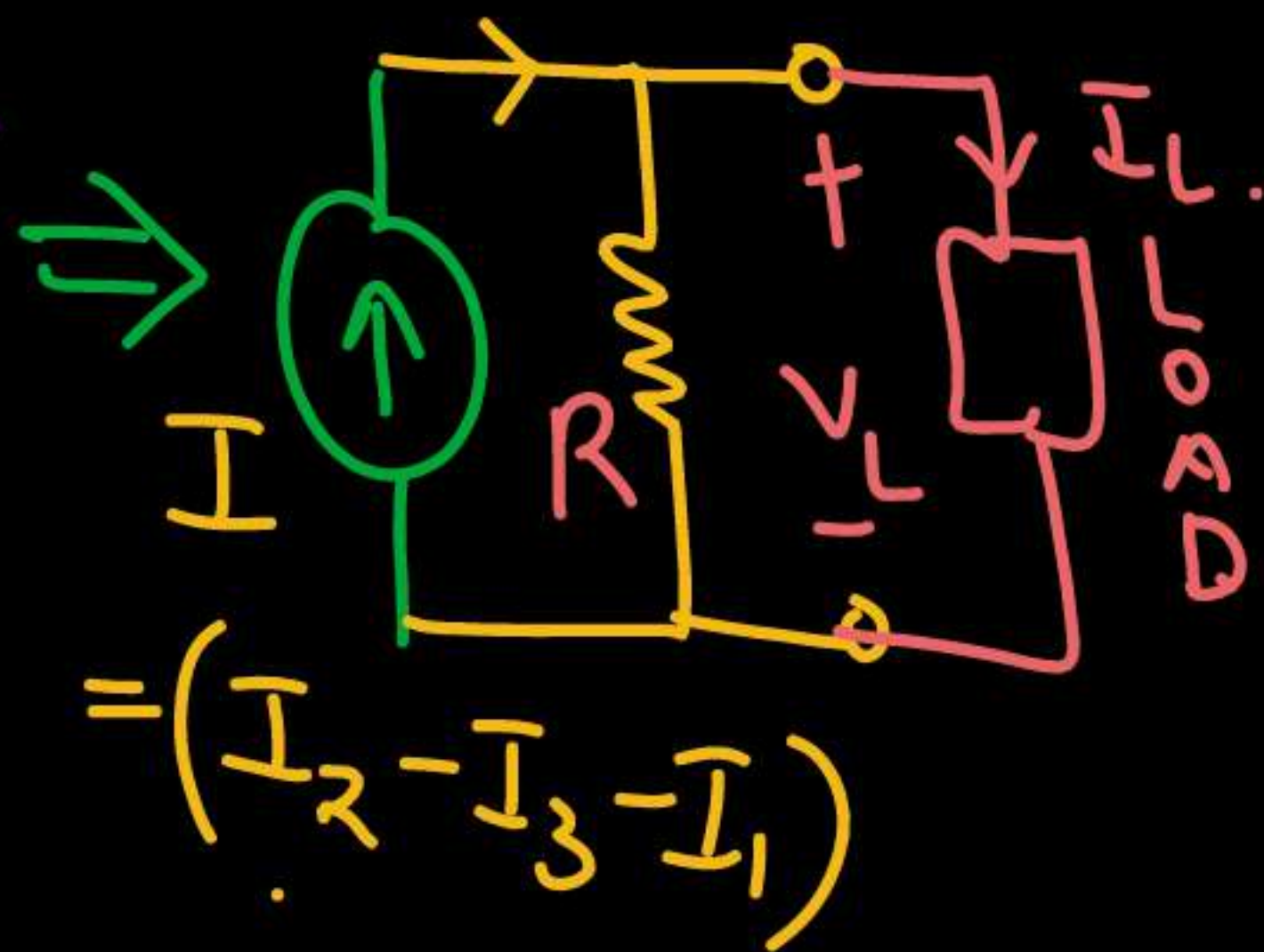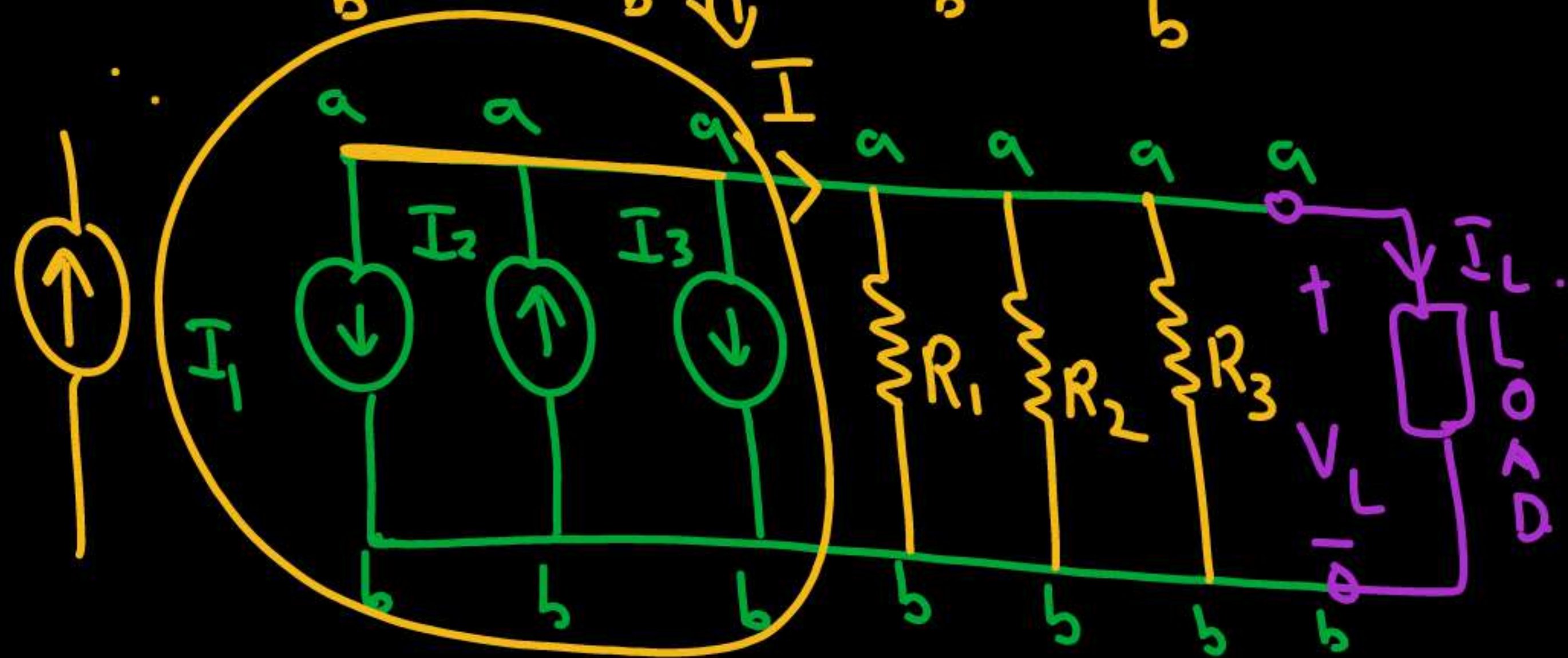
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$




[Note: ^{Imp} All the concepts of Series & Parallel operation of Independent voltage & current source are equally Applicable for Dependent voltage & current sources.]

Note: In electric Circuit.

$\left\{ \begin{array}{l} R \rightarrow \text{Always absorbs \& Dissipate Power} \\ L \rightarrow \text{By default absorbs Power} \rightarrow \text{Store energy} \\ C \rightarrow \text{By default absorbs Power} \rightarrow \text{Store energy} \end{array} \right\}$

Topic - (Nature of Element).

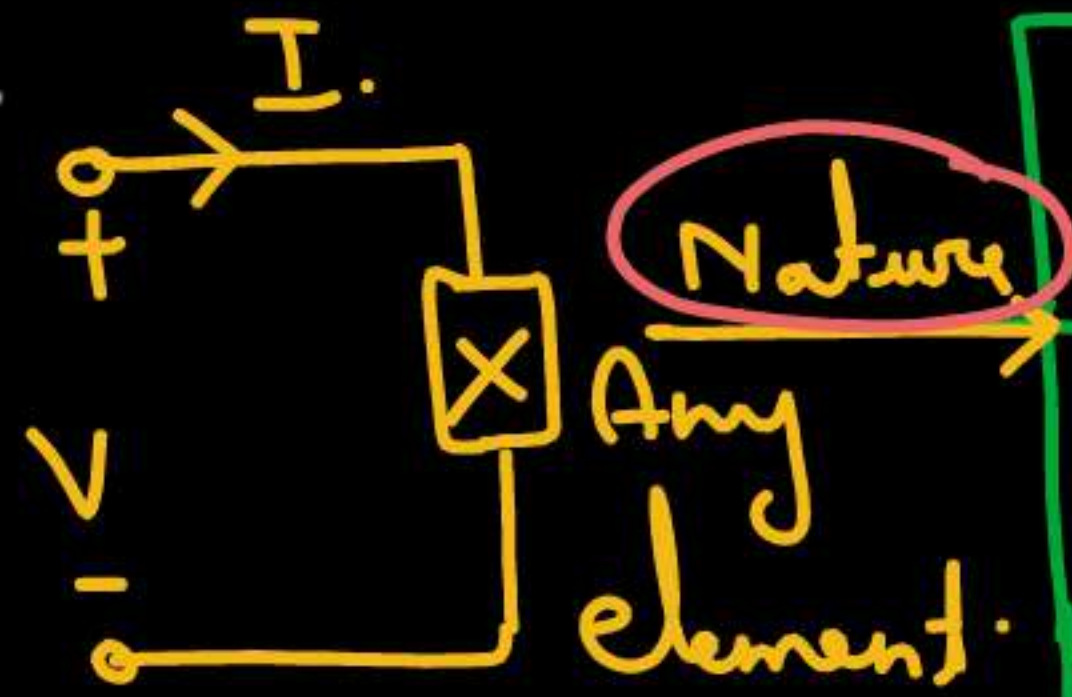

Linear or Non-linear.

Active or Passive.

Bilateral or Unilateral.

Time Variant or Time Invariant.
(TV) or (TIV).

→ These nature of element will depend upon the connection of element in circuit & also the other conditions of circuit.

Thank you

GW
Soldiers !

